 


The Intel Microprocessors

8086/8088, 80186/80188, 80286, 80386, 80486 Pentium, Pentium Pro Processor, Pentium II, Pentium 4, and Core2 with 64-bit Extensions

Architecture, Programming, and Interfacing



EIGHTH EDITION

Barry B. Brey

PEARSON

Chapter 11: Basic I/O Interface

Introduction

- This chapter outlines some of the basic methods of communications, both serial and parallel, between humans or machines and the microprocessor.
- We first introduce the basic I/O interface and discuss decoding for I/O devices.
- Then, we provide detail on parallel and serial interfacing, both of which have a variety of applications.

Chapter Objectives

Upon completion of this chapter, you will be able to:

- Explain the operation of the basic input and output interfaces.
- Decode an 8-, 16-, and 32-bit I/O device so that they can be used at any I/O port address.
- Define handshaking and explain how to use it with I/O devices.
- Interface and program the 82C55 programmable parallel interface.

Chapter Objectives

(*cont.*)

Upon completion of this chapter, you will be able to:

- Interface LCD displays, LED displays, keyboards, ADC, DAC, and various other devices to the 82C55.
- Interface and program the 16550 serial communications interface adapter.
- Interface and program the 8254 programmable interval timer.

Chapter Objectives

(*cont.*)

Upon completion of this chapter, you will be able to:

- Interface an analog-to-digital converter and a digital-to-analog converter to the microprocessor.
- Interface both DC and stepper motors to the microprocessor.

11-1 INTRO TO I/O INTERFACE

- I/O instructions (IN, INS, OUT, and OUTS) are explained.
- Also isolated (direct or I/O mapped I/O) and memory-mapped I/O, the basic input and output interfaces, and handshaking.
- Knowledge of these topics makes it easier to understand the connection and operation of the programmable interface components and I/O techniques.

The I/O Instructions

- One type of instruction transfers information to an I/O device (OUT).
- Another reads from an I/O device (IN).
- Instructions are also provided to transfer strings of data between memory and I/O.
 - INS and OUTS, found except the 8086/8088

- Instructions that transfer data between an I/O device and the microprocessor's accumulator (AL, AX, or EAX) are called **IN** and **OUT**.
- The I/O address is stored in register DX as a 16-bit address or in the byte (p8) immediately following the opcode as an 8-bit address.
 - Intel calls the 8-bit form (p8) a **fixed address** because it is stored with the instruction, usually in a ROM
- The 16-bit address is called a **variable address** because it is stored in a DX, and then used to address the I/O device.

- Other instructions that use DX to address I/O are the INS and OUTS instructions.
- I/O ports are 8 bits in width.
 - a 16-bit port is actually two consecutive 8-bit ports being addressed
 - a 32-bit I/O port is actually four 8-bit ports

- When data are transferred using IN or OUT, the I/O address, (**port number** or simply port), appears on the address bus.
- External I/O interface decodes the port number in the same manner as a memory address.
 - the 8-bit fixed port number (p8) appears on address bus connections A_7 – A_0 with bits A_{15} – A_8 equal to 00000000_2
 - connections above A_{15} are undefined for I/O instruction

- The 16-bit variable port number (DX) appears on address connections A_{15} – A_0 .
- The first 256 I/O port addresses (00H–FFH) are accessed by both fixed and variable I/O instructions.
 - any I/O address from 0100H to FFFFH is only accessed by the variable I/O address
- In a PC computer, all 16 address bus bits are decoded with locations 0000H–03FFH.
 - used for I/O inside the PC on the ISA (**industry standard architecture**) bus

- INS and OUTS instructions address an I/O device using the DX register.
 - but do not transfer data between accumulator and I/O device as do the IN/OUT instructions
 - Instead, they transfer data between memory and the I/O device
- Pentium 4 and Core2 operating in the 64-bit mode have the same I/O instructions.
- There are no 64-bit I/O instructions in the 64-bit mode.
 - most I/O is still 8 bits and likely will remain so

Isolated and Memory-Mapped I/O



- Two different methods of interfacing I/O: **isolated I/O** and **memory-mapped I/O**.
- In isolated I/O, the IN, INS, OUT, and OUTS transfer data between the microprocessor's accumulator or memory and the I/O device.
- In memory-mapped I/O, any instruction that references memory can accomplish the transfer.
- The PC does not use memory-mapped I/O.

Isolated I/O

- The most common I/O transfer technique used in the Intel-based system is isolated I/O.
 - *isolated* describes how I/O locations are isolated from memory in a separate I/O address space
- Addresses for isolated I/O devices, called ports, are separate from memory.
- Because the ports are separate, the user can expand the memory to its full size without using any of memory space for I/O devices.

- A disadvantage of isolated I/O is that data transferred between I/O and microprocessor must be accessed by the IN, INS, OUT, and OUTS instructions.
- Separate control signals for the I/O space are developed (using M/\overline{IO} and W/\overline{R}), which indicate an I/O read (\overline{IORC}) or an I/O write (\overline{RD}) operation.
- These signals indicate an I/O port address, which appears on the address bus, is used to select the I/O device.

Figure 11–1 The memory and I/O maps for the 8086/8088 microprocessors. (a) Isolated I/O. (b) Memory-mapped I/O.

  


- in the PC, isolated I/O ports are used to control peripheral devices
- an 8-bit port address is used to access devices located on the system board, such as the timer and keyboard interface
- a 16-bit port is used to access serial and parallel ports, video and disk drive systems

Memory-Mapped I/O

- Memory-mapped I/O does not use the IN, INS, OUT, or OUTS instructions.
- It uses any instruction that transfers data between the microprocessor and memory.
 - treated as a memory location in memory map
- Advantage is any memory transfer instruction can access the I/O device.
- Disadvantage is a portion of memory system is used as the I/O map.
 - reduces memory available to applications

Personal Computer I/O Map

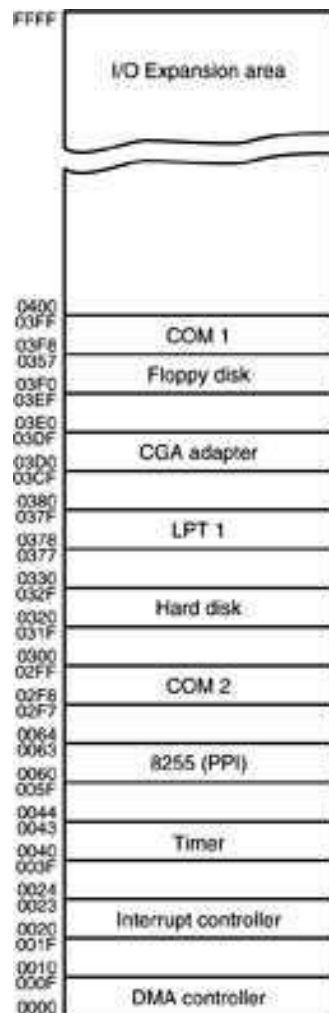

- the PC uses part of I/O map for dedicated functions, as shown here
- I/O space between ports 0000H and 03FFH is normally reserved for the system and ISA bus
- ports at 0400H–FFFFH are generally available for user applications, main-board functions, and the PCI bus
- 80287 coprocessor uses 00F8H–00FFH, so Intel reserves I/O ports 00F0H–00FFH

Figure 11–2 I/O map of a personal computer illustrating many of the fixed I/O areas.


Basic Input and Output Interfaces

- The basic input device is a set of three-state buffers.
- The basic output device is a set of data latches.
- The term IN refers to moving data *from* the I/O device *into* the microprocessor and
- The term OUT refers to moving data *out* of the microprocessor *to* the I/O device.

The Basic Input Interface

- Three-state buffers are used to construct the 8-bit input port depicted in Figure 11–3.
- External TTL data are connected to the inputs of the buffers.
 - buffer outputs connect to the data bus
- The circuit of allows the processor to read the contents of the eight switches that connect to any 8-bit section of the data bus when the select signal becomes a logic 0.

Figure 11–3 The basic input interface illustrating the connection of eight switches. Note that the 74ALS244 is a three-state buffer that controls the application of the switch data to the data bus.

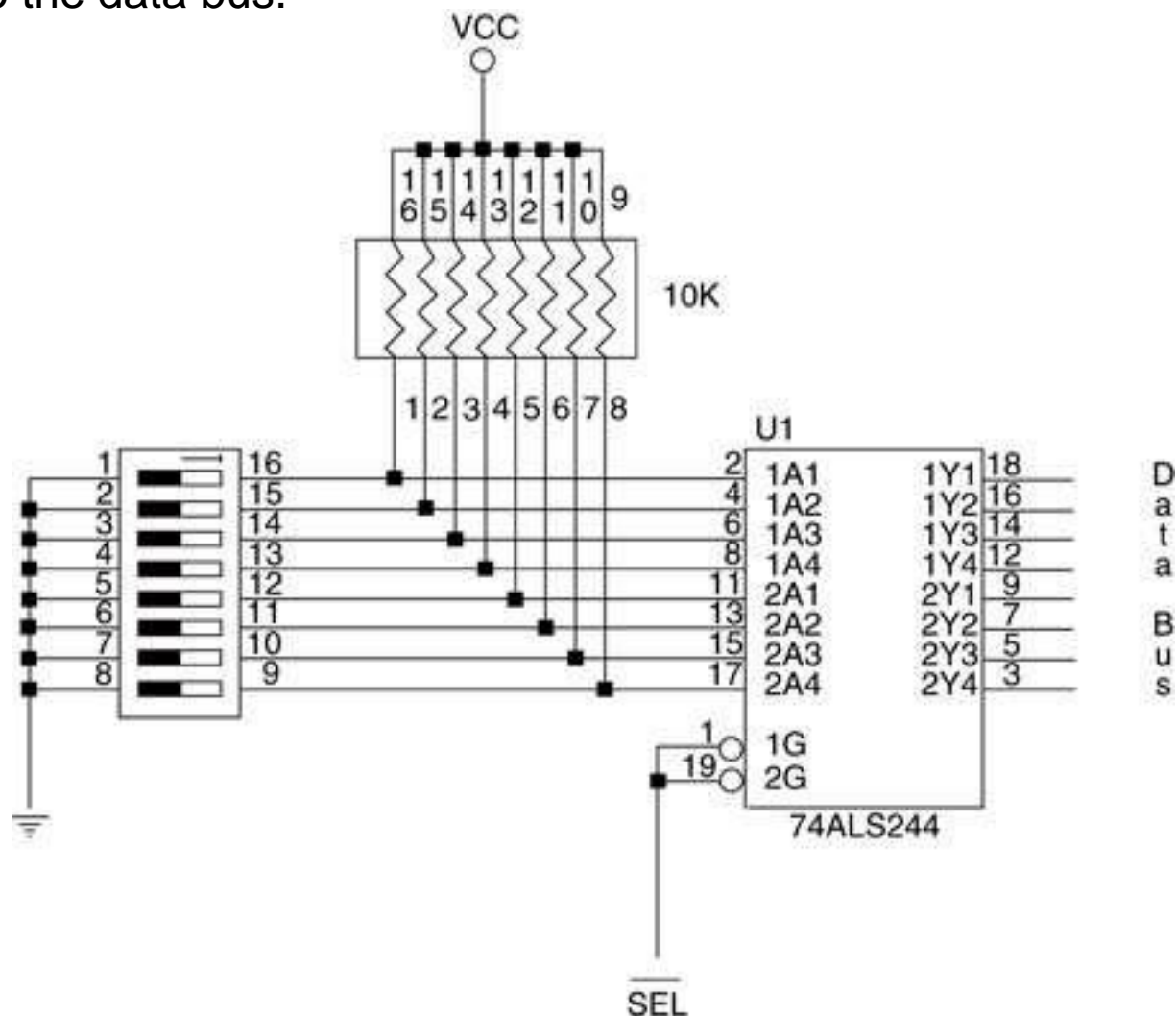


- When the IN instruction executes, contents of the switches copy to the AL register.
- This basic input circuit is not optional and must appear any time input data are interfaced to the microprocessor.
- Sometimes it appears as a discrete part of the circuit, as shown in Figure 11–3.
 - also built into a programmable I/O devices
- Sixteen- or 32-bit data can also be interfaced but is not nearly as common as 8-bit data.

The Basic Output Interface

- Receives data from the processor and usually must hold it for some external device.
 - latches or flip-flops, like buffers in the input device, are often built into the I/O device
- Fig 11–4 shows how eight light-emitting diodes (LEDs) connect to the processor through a set of eight data latches.
- The latch stores the number output by the microprocessor from the data bus so that the LEDs can be lit with any 8-bit binary number.

Figure 11–4 The basic output interface connected to a set of LED displays.

 


- Latches hold the data because when the processor executes an OUT, data are only present on the data bus for less than $1.0\ \mu\text{s}$.
 - the viewer would never see the LEDs illuminate
- When the OUT executes, data from AL, AX, or EAX transfer to the latch via the data bus.
- Each time the OUT executes, the $\overline{\text{SEL}}$ signal activates, capturing data to the latch.
 - data are held until the next OUT
- When the output instruction is executed, data from the AL register appear on the LEDs.

Handshaking

- Many I/O devices accept or release information slower than the microprocessor.
- A method of I/O control called **handshaking** or **polling**, synchronizes the I/O device with the microprocessor.
- An example is a parallel printer that prints a few hundred characters per second (CPS).
- The processor can send data much faster.
 - a way to slow the microprocessor down to match speeds with the printer must be developed

- Fig 11–5 illustrates typical input and output connections found on a printer.
 - data transfers via data connections (D_7 – D_0)
- ASCII data are placed on D_7 – D_0 , and a pulse is then applied to the \overline{STB} connection.
 - BUSY indicates the printer is busy
 - \overline{STB} is a clock pulse used to send data to printer
- The strobe signal sends or clocks the data into the printer so that they can be printed.
 - as the printer receives data, it places logic 1 on the BUSY pin, indicating it is printing data

Figure 11–5 The DB25 connector found on computers and the Centronics 36-pin connector found on printers for the Centronics parallel printer interface.

 

DB25 Pin number	CENT36 Pin number	Function	DB25 Pin number	CENT36 Pin number	Function
1	1	Data Strobe	12	12	Paper empty
2	2	Data 0 (D0)	13	13	Select
3	3	Data 1 (D1)	14	14	Afd
4	4	Data 2 (D2)	15	32	Error
5	5	Data 3 (D3)	16	—	RESET
6	6	Data 4 (D4)	17	31	Select in
7	7	Data 5 (D5)	18–25	19–30	Ground
8	8	Data 6 (D6)	—	17	Frame ground
9	9	Data 7 (D7)	—	16	Ground
10	10	Ack	—	33	Ground
11	11	Busy			

- The software polls or tests the BUSY pin to decide whether the printer is busy.
 - If the printer is busy, the processor waits
 - if not, the next ASCII character goes to the printer
- This process of interrogating the printer, or any asynchronous device like a printer, is called handshaking or polling.

11-2 I/O PORT ADDRESS DECODING

- Very similar to memory address decoding, especially for memory-mapped I/O devices.
- The difference between memory decoding and isolated I/O decoding is the number of address pins connected to the decoder.
- In the personal computer system, we always decode all 16 bits of the I/O port address.

Decoding 8-Bit I/O Port Addresses

- Fixed I/O instruction uses an 8-bit I/O port address that on $A_{15}-A_0$ as 0000H–00FFH.
 - we often decode only address connections A_7-A_0 for an 8-bit I/O port address
- The DX register can also address I/O ports 00H–FFH.
- If the address is decoded as an 8-bit address, we can never include I/O devices using a 16-bit address.
 - the PC never uses or decodes an 8-bit address

- Figure 11–10 shows a 74ALS138 decoder that decodes 8-bit I/O ports F0H - F7H.
 - identical to a memory address decoder except we only connect address bits A_7 – A_0 to the inputs of the decoder
- Figure 11–11 shows the PLD version, using a GAL22V10 (a low-cost device) for this decoder.
- The PLD is a better decoder circuit because the number of integrated circuits has been reduced to one device.

Figure 11–10 A port decoder that decodes 8-bit I/O ports. This decoder generates active low outputs for ports F0H–F7H.


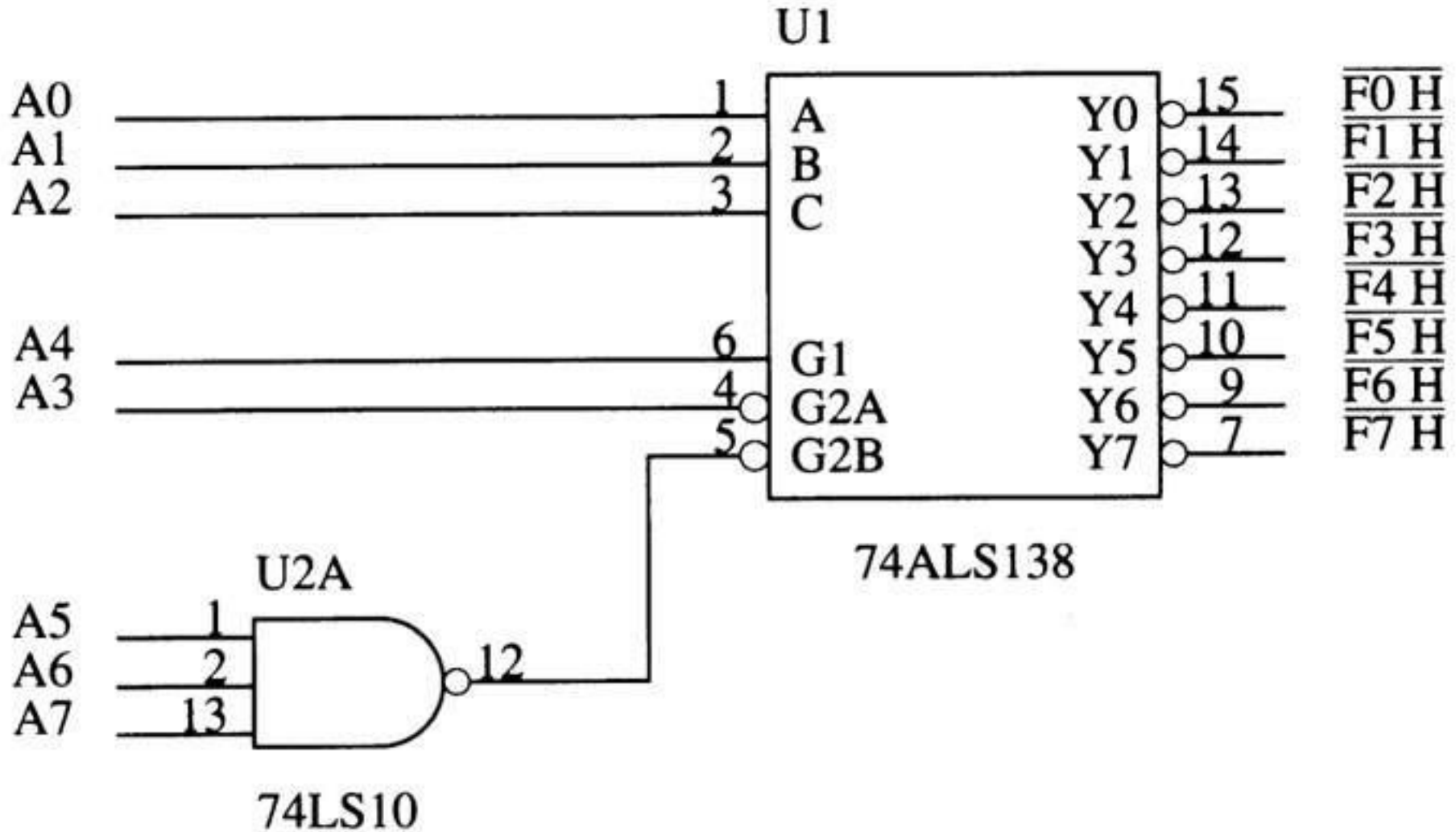



Figure 11–11 A PLD that generates part selection signals

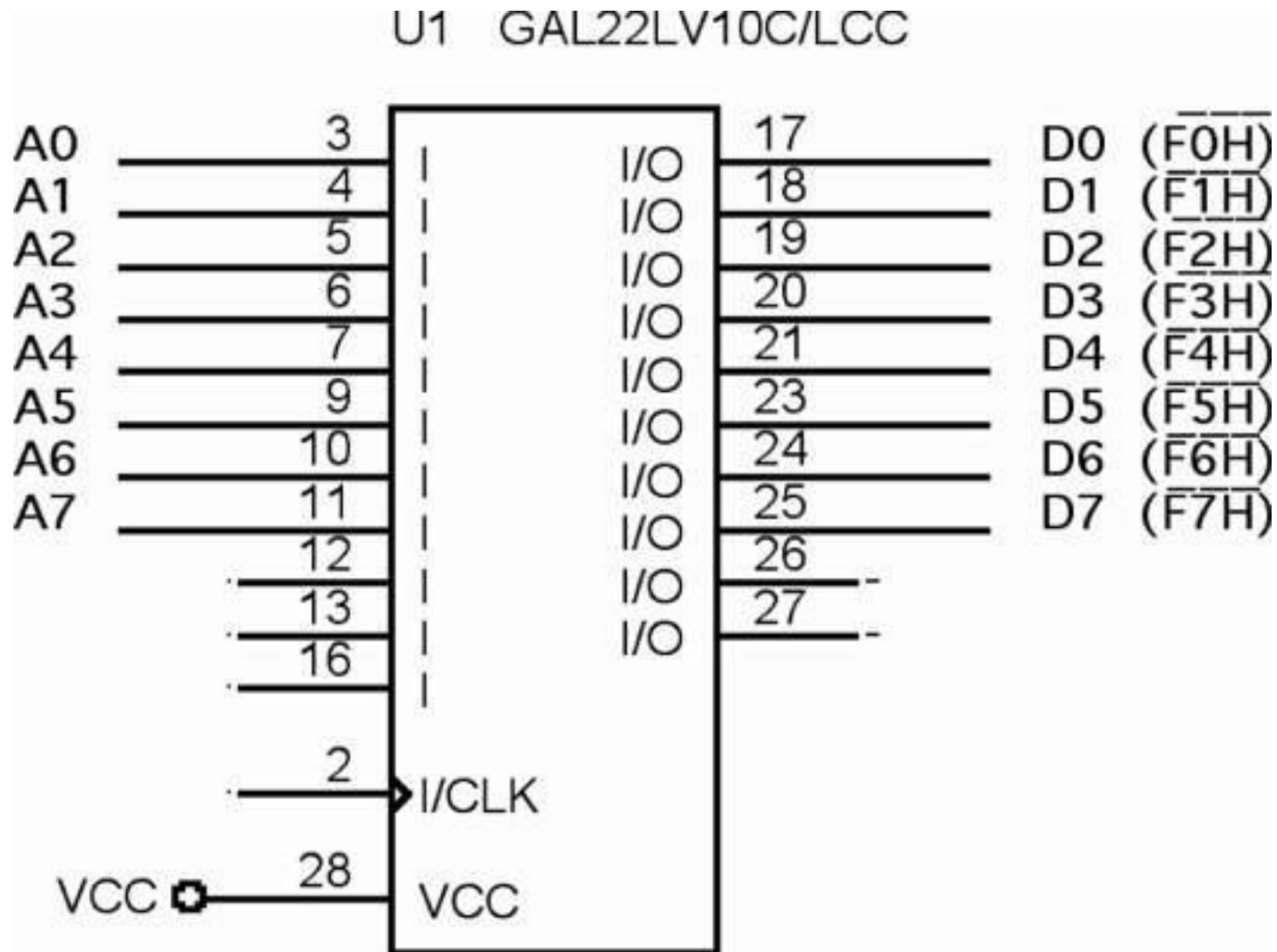

Decoding 16-Bit I/O Port Addresses

- PC systems typically use 16-bit I/O addresses.
 - 16-bit addresses rare in embedded systems
- The difference between decoding an 8-bit and a 16-bit I/O address is that eight additional address lines (A_{15} – A_8) must be decoded.
- Figure 11–12 illustrates a circuit that contains a PLD and a 4-input NAND gate used to decode I/O ports EFF8H–EFFFH.
- PLD generates address strobes for I/O ports


Figure 11–12 A PLD that decodes 16-bit I/O ports EFF8H through EFFFH.

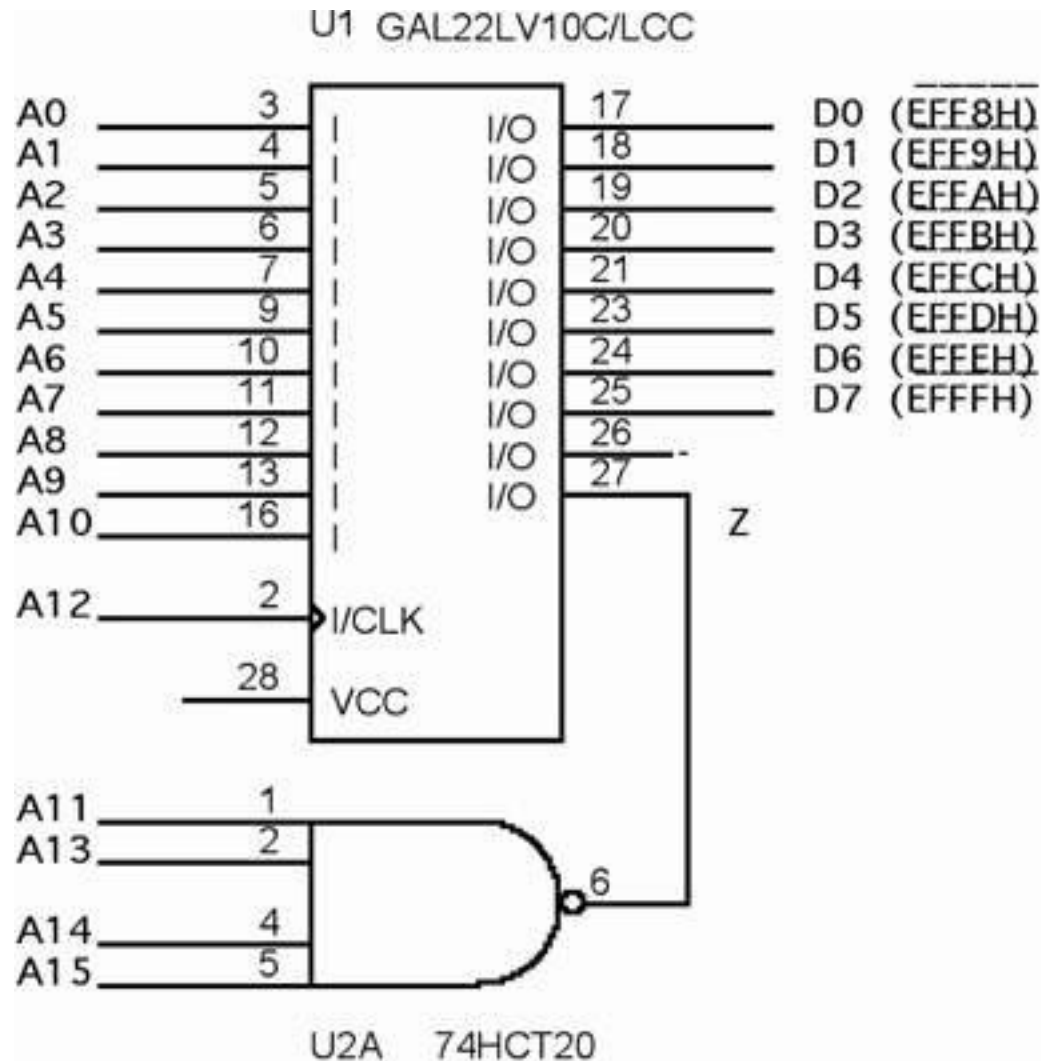

8- and 16-Bit Wide I/O Ports


- Data transferred to an 8-bit I/O device exist in one of the I/O banks in a 16-bit processor such as 80386SX.
- The I/O system on such a microprocessor contains two 8-bit memory banks.
- Fig 11–13 shows separate I/O banks for a 16-bit system such as 80386SX.
- Because two I/O banks exist, any 8-bit I/O write requires a separate write.

Figure 11–13 The I/O banks found in the 8086, 80186, 80286, and 80386SX.

 

- I/O reads don't require separate strobes.
 - as with memory, the processor reads only the byte it expects and ignores the other byte
 - a read can cause problems when an I/O device responds incorrectly to a read operation
- Fig 11–14 shows a system with two different 8-bit output devices, located at 40H and 41H.
- These are 8-bit devices and appear in different I/O banks.
 - thus, separate I/O write signals are generated to clock a pair of latches that capture port data


Figure 11–14 An I/O port decoder that selects ports 40H and 41H for output data.

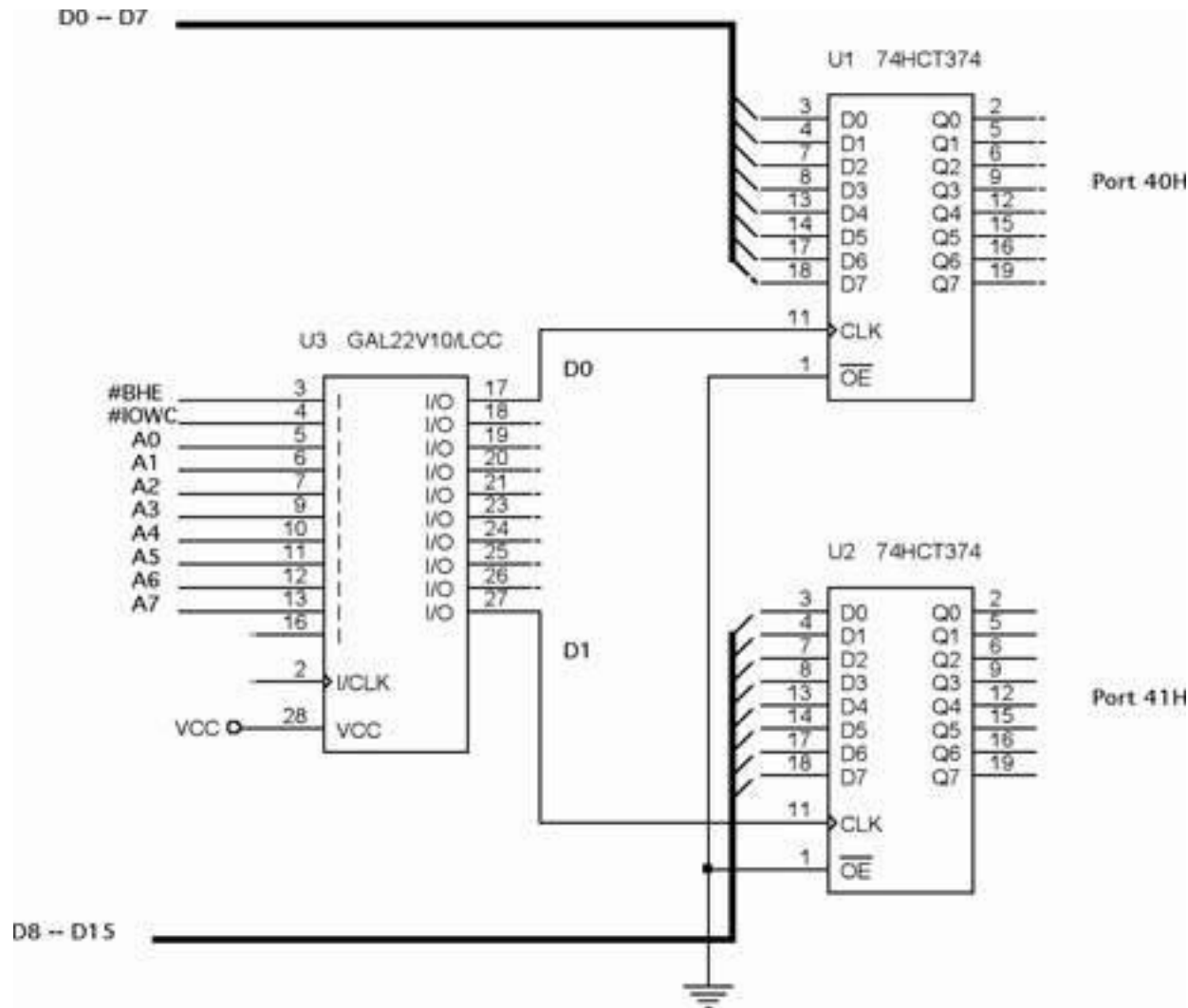

- all I/O ports use 8-bit addresses
- ports 40H & 41H can be addressed as separate 8-bit ports
- or as one 16-bit port

- Fig 11–15 shows a 16-bit device connected to function at 8-bit addresses 64H & 65H.
- The PLD decoder does not have a connection for address bits $\overline{\text{BLE}}$ (A_0) and $\overline{\text{BHE}}$ because the signals don't apply to 16-bit-wide devices.
- The program for the PLD, illustrated in Example 11–5, shows how the enable signals are generated for the three-state buffers (74HCT244) used as input devices.


Figure 11–15 A 16-bit-wide port decoded at I/O addresses 64H and 65H.

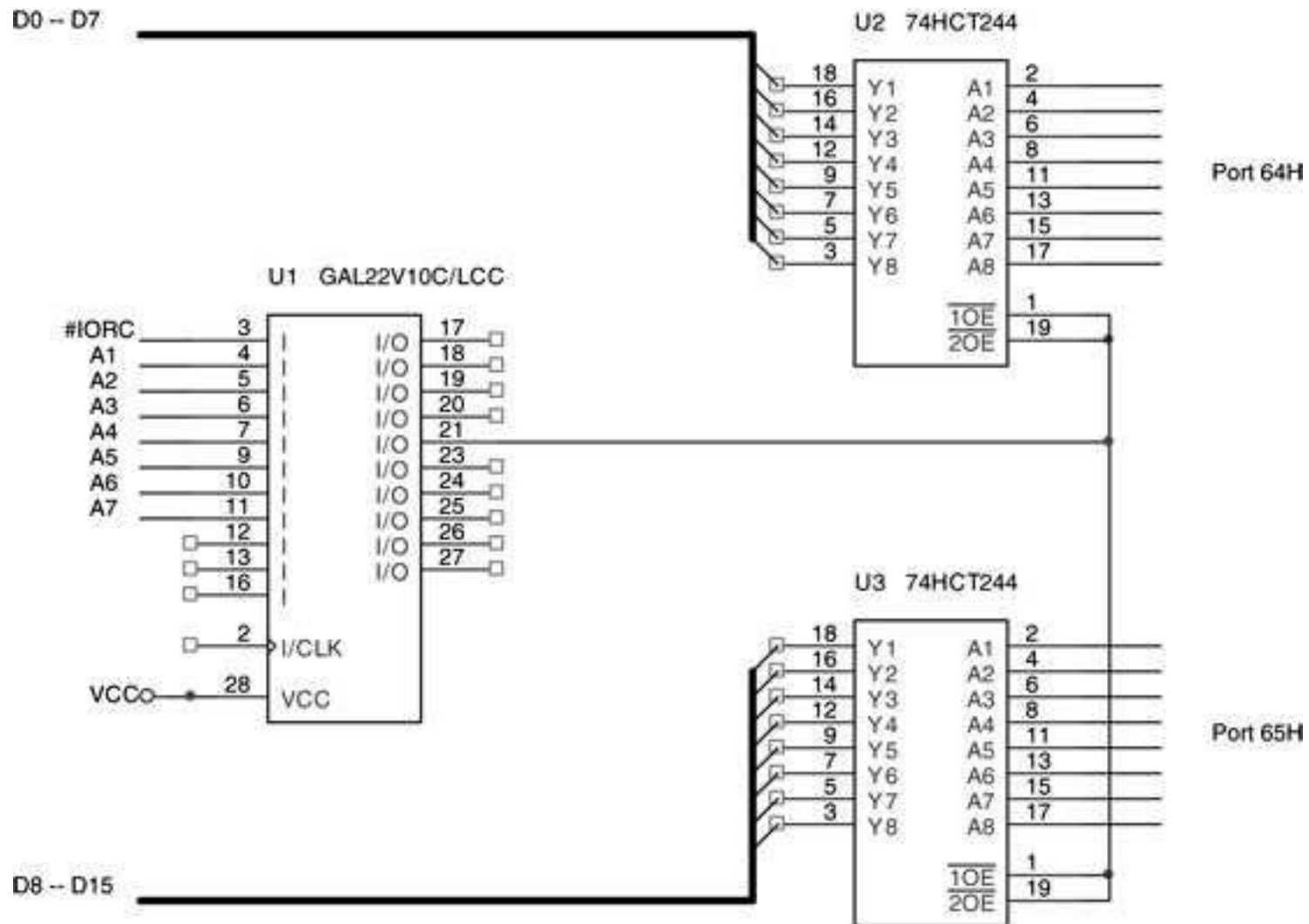

32-Bit-Wide I/O Ports

- May eventually become common because of newer buses found in computer systems.
- The EISA system bus supports 32-bit I/O as well as the VESA local and current PCI bus.
 - not many I/O devices are 32 bits in width
- Fig 11–16 shows a 32-bit input port for 80386DX - 80486DX microprocessor.
- The circuit uses a single PLD to decode the I/O ports and four 74HCT244 buffers to connect the I/O data to the data bus.

Figure 11–16 A 32-bit-wide port decoded at 70H through 73H for the 80486DX microprocessor.

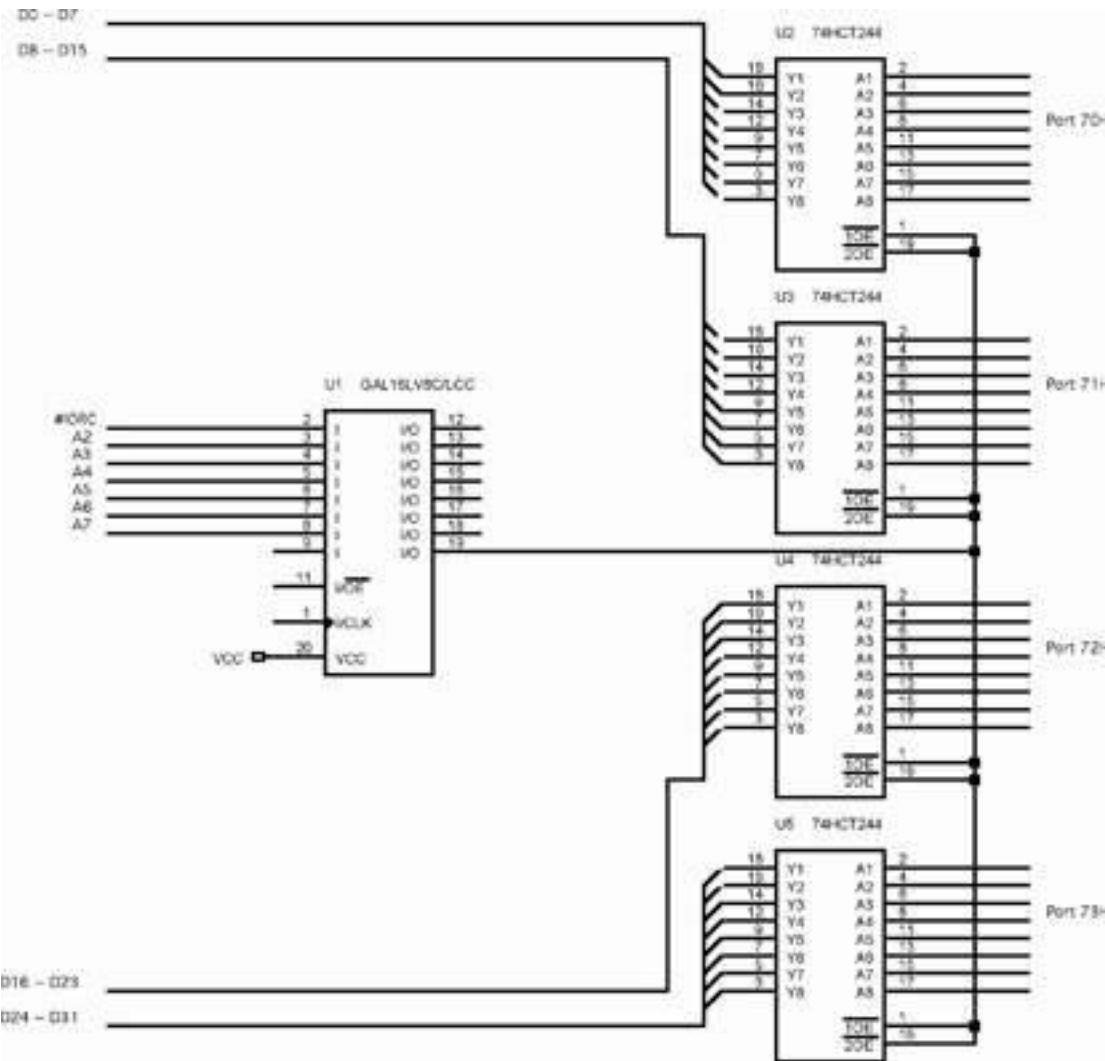


- I/O ports decoded by this interface are the 8-bit ports 70H–73H
- When writing to access this port, it is crucial to use the address 70H for 32-bit input
- as instruction `IN EAX, 70H`

- With the Pentium–Core2 and their 64-bit data buses, I/O ports appear in various banks, as determined by the I/O port address.
- A 32-bit I/O access in the Pentium system can appear in any four consecutive I/O banks.
 - 32-bit ports 0100H–0103H appear in banks 0–3
- I/O address range must begin at a location where the rightmost two bits are zeros.
 - 0100H–0103H is allowable
 - 0101H–0104H is not

- Widest I/O transfers are 32 bits, and there are no I/O instructions to support 64-bit transfers.
 - true for Pentium 4 or Core2 in the 64-bit mode
- Suppose we need to interface a 16-bit-wide output port at I/O address 2000H and 2001H.
 - interface is illustrated in Figure 11–17
 - PLD program is listed in Example 11–7
- The problem that can arise is when the I/O port spans across a 64-bit boundary.
 - example, a 16-bit- port at 2007H and 2008H

Figure 11–17 A Pentium 4 interfaced to a 16-bit-wide I/O port at port addresses 2000H and 2001H.

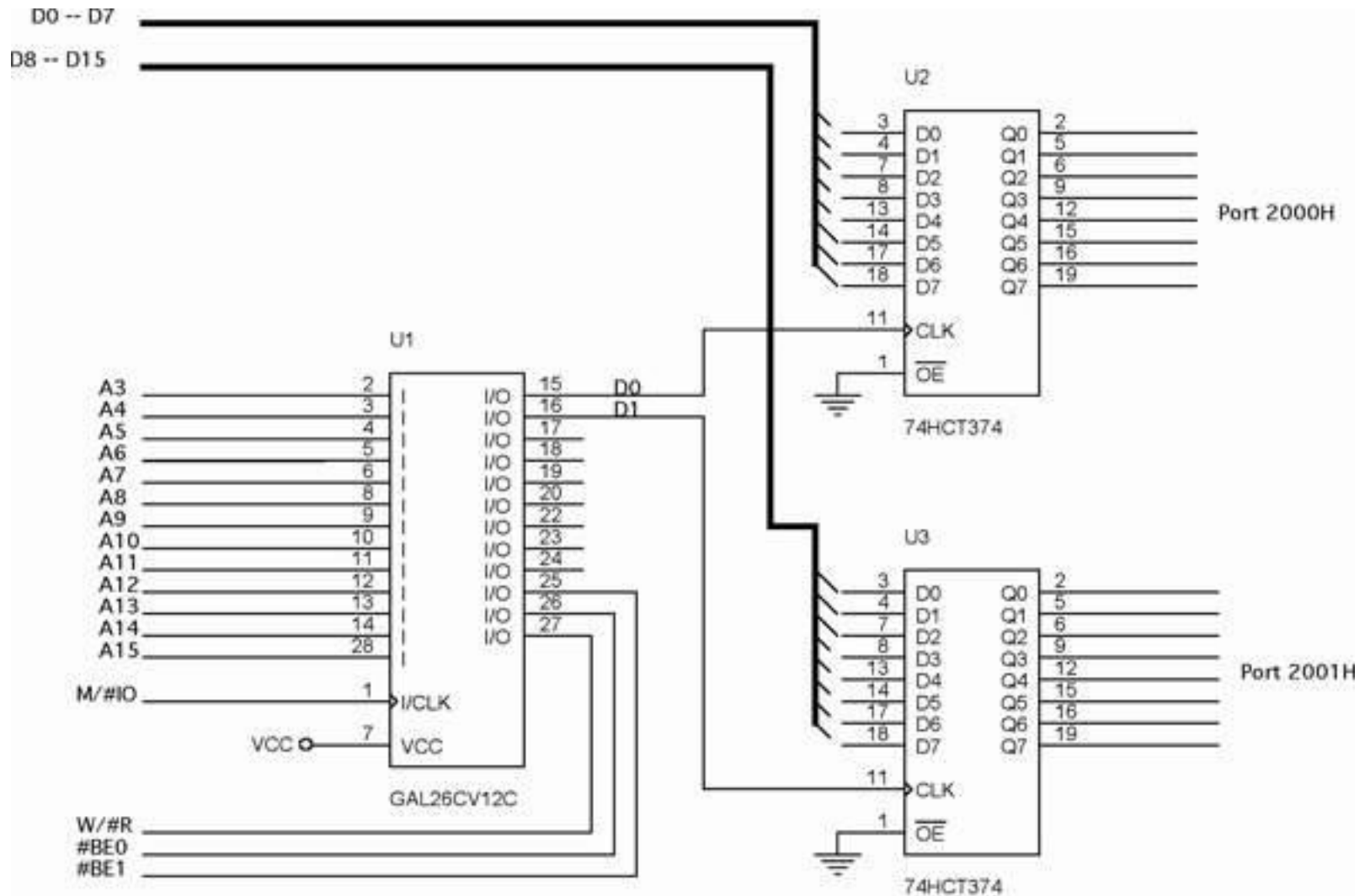

11–3 THE PROGRAMMABLE PERIPHERAL

- **82C55 programmable peripheral interface (PPI)** is a popular, low-cost interface component found in many applications.
- The PPI has 24 pins for I/O, programmable in groups of 12 pins and groups that operate in three distinct modes of operation.
- 82C55 can interface any TTL-compatible I/O device to the microprocessor.


- The 82C55 (CMOS version) requires wait states if operated with a processor using higher than an 8 MHz clock.
 - also provides at least 2.5 mA of sink (logic 0) current at each output, a maximum of 4.0 mA
- Because I/O devices are inherently slow, wait states used during I/O transfers do not impact significantly upon the speed of the system.
- The 82C55 still finds application even in the latest Core2-based computer system.

- 82C55 is used for interface to the keyboard and parallel printer port in many PCs.
 - found as a function within an interfacing chip set
 - also controls the timer and reads data from the keyboard interface
- An experimentation board is available that plugs into the parallel port of a PC, to allow access to an 8255 located on the board.
- The 8255 is programmed in either assembly language or Visual C++ through drivers available with the board.

Basic Description of the 82C55

- Fig 11–18 shows pin-outs of the 82C55 in DIP and surface mount (flat pack) format.
- The three I/O ports (labeled A, B, and C) are programmed as groups.
 - group A connections consist of port A (PA_7 – PA_0) and the upper half of port C (PC_7 – PC_4)
 - group B consists of port B (PB_7 – PB_0) and the lower half of port C (PC_3 – PC_0)
- 82C55 is selected by its \overline{CS} pin for programming and reading/writing to a port.


Figure 11–18 The pin-out of the 82C55 peripheral interface adapter (PPI).

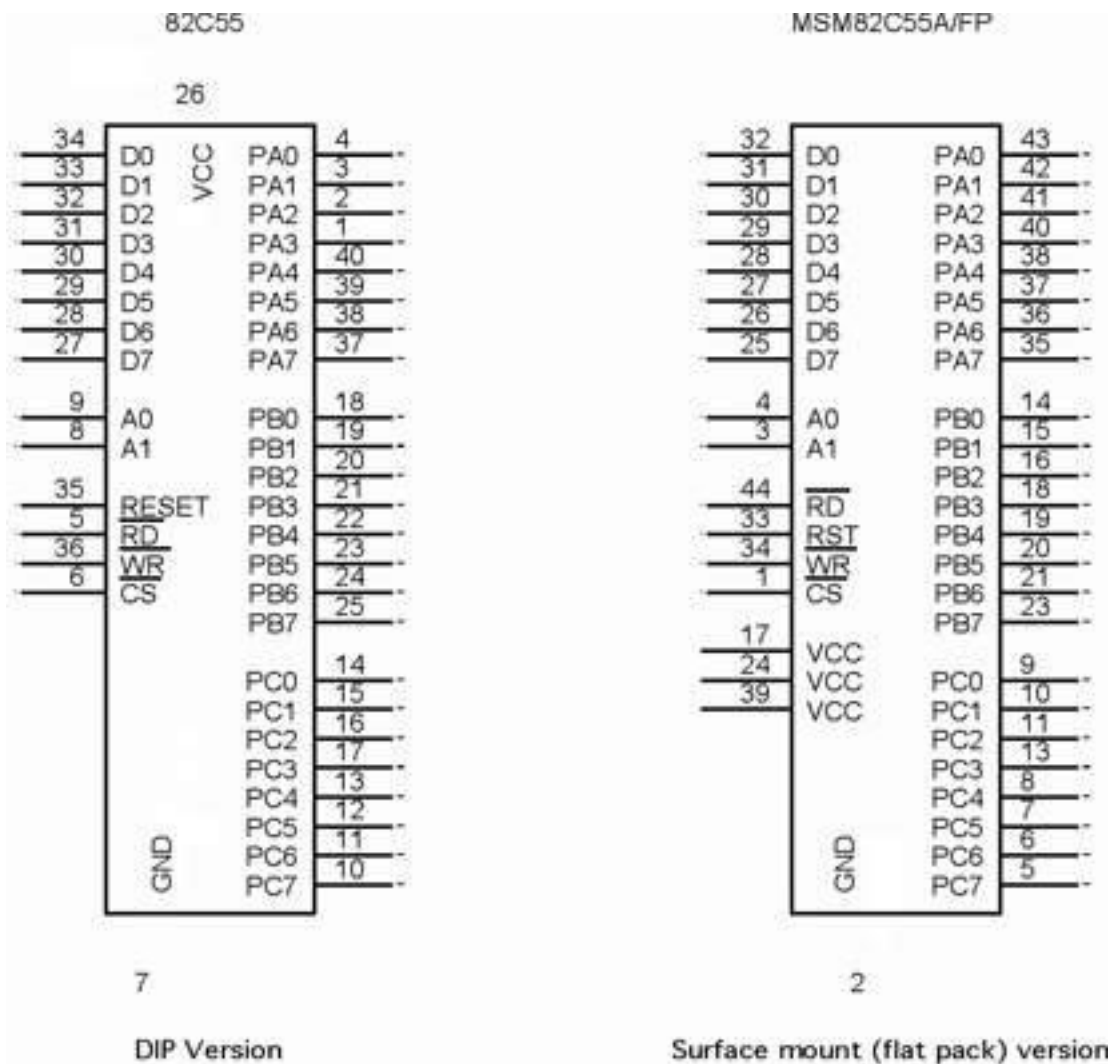

- Table 11–2 shows I/O port assignments used for programming and access to the I/O ports.
- In the PC, a pair of 82C55s, or equivalents, are decoded at I/O ports 60H–63H and also at ports 378H–37BH.
- The 82C55 is a fairly simple device to interface to the microprocessor and program.
- For 82C55 to be read or written, the \overline{CS} input must be logic 0 and the correct I/O address must be applied to the A_1 and A_0 pins.
- Remaining port address pins are *don't cares*.

- Fig 11–19 shows an 82C55 connected to the 80386SX so it functions at 8-bit addresses C0H (port A), C2H (port B), C4H (port C), and C6H (command register).
 - this interface uses the low bank of the I/O map
- All 82C55 pins are direct connections to the 80386SX, except the \overline{CS} pin. The pin is decoded/selected by a 74ALS138 decoder.
- A RESET to 82C55 sets up all ports as simple input ports using mode 0 operation.
 - initializes the device when the processor is reset

Figure 11–19 The 82C55 interfaced to the low bank of the 80386SX microprocessor.

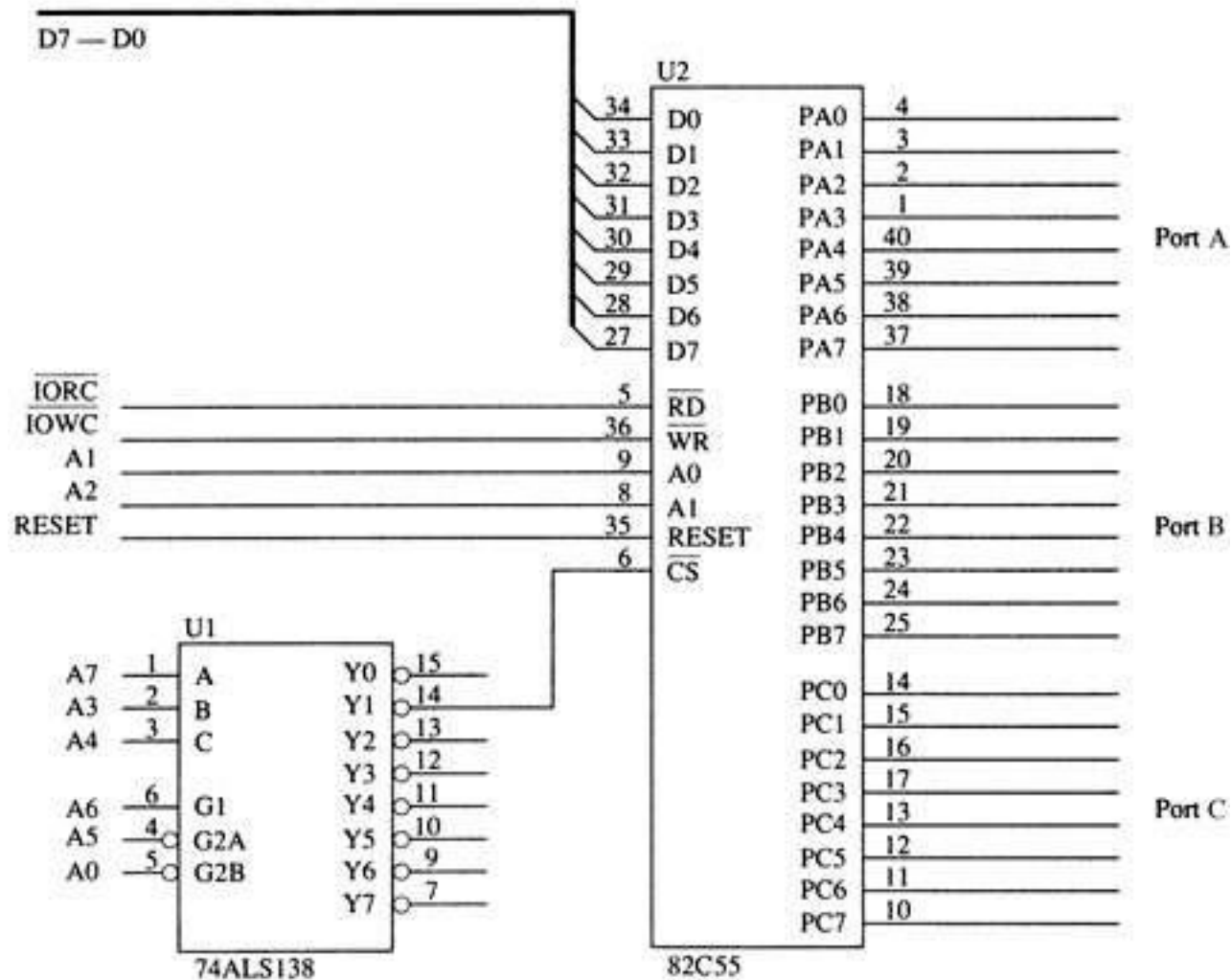


- After a RESET, no other commands are needed, as long as it is used as an input device for all three ports.
- 82C55 is interfaced to the PC at port addresses 60H–63H for keyboard control.
 - also for controlling the speaker, timer, and other internal devices such as memory expansion
- It is also used for the parallel printer port at I/O ports 378H–37BH.

Programming the 82C55

- 82C55 is programmed through two internal command registers shown in Figure 11–20.
- Bit position 7 selects either command byte A or command byte B.
 - command byte A programs functions of group A and B
 - byte B sets (1) or resets (0) bits of port C only if the 82C55 is programmed in mode 1 or 2
- Group B (port B and the lower part of port C) are programmed as input or output pins.

Figure 11–20 The command byte of the command register in the 82C55. (a) Programs ports A, B, and C. (b) Sets or resets the bit indicated in the select a bit field.

 


- group B operates in mode 0 or mode 1
- mode 0 is basic input/output mode that allows the pins of group B to be programmed as simple input and latched output connections
- Mode 1 operation is the strobed operation for group B connections
- data are transferred through port B
- handshaking signals are provided by port C

- Group A (port A and the upper part of port C) are programmed as input or output pins.
- Group A can operate in modes 0, 1, and 2.
 - mode 2 operation is a bidirectional mode of operation for port A
- If a 0 is placed in bit position 7 of the command byte, command byte B is selected
- This allows any bit of port C to be set (1) or reset (0), if the 82C55 is operated in either mode 1 or 2.
 - otherwise, this byte is not used for programming

Mode 0 Operation

- Mode 0 operation causes 82C55 to function:
 - as a buffered input device
 - as a latched output device
- Fig 11–21 shows 82C55 connected to a set of eight seven-segment LED displays.
- These are standard LEDs.
 - the interface can be modified with a change in resistor values for an organic LED (OLED) display or high-brightness LEDs

Figure 11–21 An 8-digit LED display interfaced to the 8088 microprocessor through an 82C55 PIA.

 

- ports A & B are programmed as (mode 0) simple latched output ports
- port A provides segment data inputs
port B provides a means of selecting one display position at a time for multiplexing the displays
- the 82C55 is interfaced to an 8088 through a PLD so it functions at I/O port numbers 0700H–0703H
- PLD decodes the I/O address and develops the write strobe for the \overline{WR} pin of the 82C55


- Resistor values in Fig 11–21 are chosen so the segment current is 80 mA.
 - required to produce average 10 mA current per segment as the displays are multiplexed
- A six-digit display uses a segment current of 60 mA for an average of 10 mA per segment.
- Peak anode current in an eight-digit display is 560 mA (seven segments \times 80 mA).
 - average anode current is 80 mA
- In a six-digit display, peak current would be 420 mA (seven segments \times 60 mA).

- In this display, the segment load resistor passes 80 mA current and has approximately 3.0 V across it.
- The value of the resistor is $3.0 \text{ V} \div 180 \text{ mA} = 37.5 \text{ Ohm}$. The closest standard resistor value of 39 Ohm is used in Fig11–21.
- Programming the 82C55 is accomplished by the short sequence of instructions listed in Example 11–9.
- Ports A and B are programmed as outputs.

Mode 1 Strobed Input

- Causes port A and/or port B to function as latching input devices.
 - allows external data to be stored to the port until the microprocessor is ready to retrieve it
- Port C is used in mode 1 operation—not for data, but for control or handshaking signals.
 - to help operate either or both port A and B as strobed input ports
- Fig 11–27 shows how both ports are structured for mode 1 strobed input operation.

Figure 11–27 Strobed input operation (mode 1) of the 82C55. (a) Internal structure and (b) timing diagram.

 

Signal Definitions for Mode 1

Strobed Input

STB

- The **strobe** input loads data to the port latch, which holds the information until it is input to the microprocessor via the IN instruction.

IBF

- **Input buffer full** is an output indicating that the input latch contains information.

INTR

- **Interrupt request** is an output that requests an interrupt. The INTR pin becomes a logic 1 when \overline{STB} returns to a logic 1. Cleared when data are input from the port by the processor.

INTE

- **Interrupt enable signal** is neither input nor output; it is an internal bit programmed via port PC_4 (port A) or PC_2 (port B) bit position.


PC₇, PC₆

- The port C pins 7 and 6 are general-purpose I/O pins that are available for any purpose.

Strobed Input Example

- An example of a strobed input device is a keyboard.
- The keyboard encoder debounces the key switches and provides a strobe signal whenever a key is depressed.
 - the data output contains ASCII-coded key code
- Figure 11–28 illustrates a keyboard connected to strobed input port A.


Figure 11–28 Using the 82C55 for strobed input operation of a keyboard.

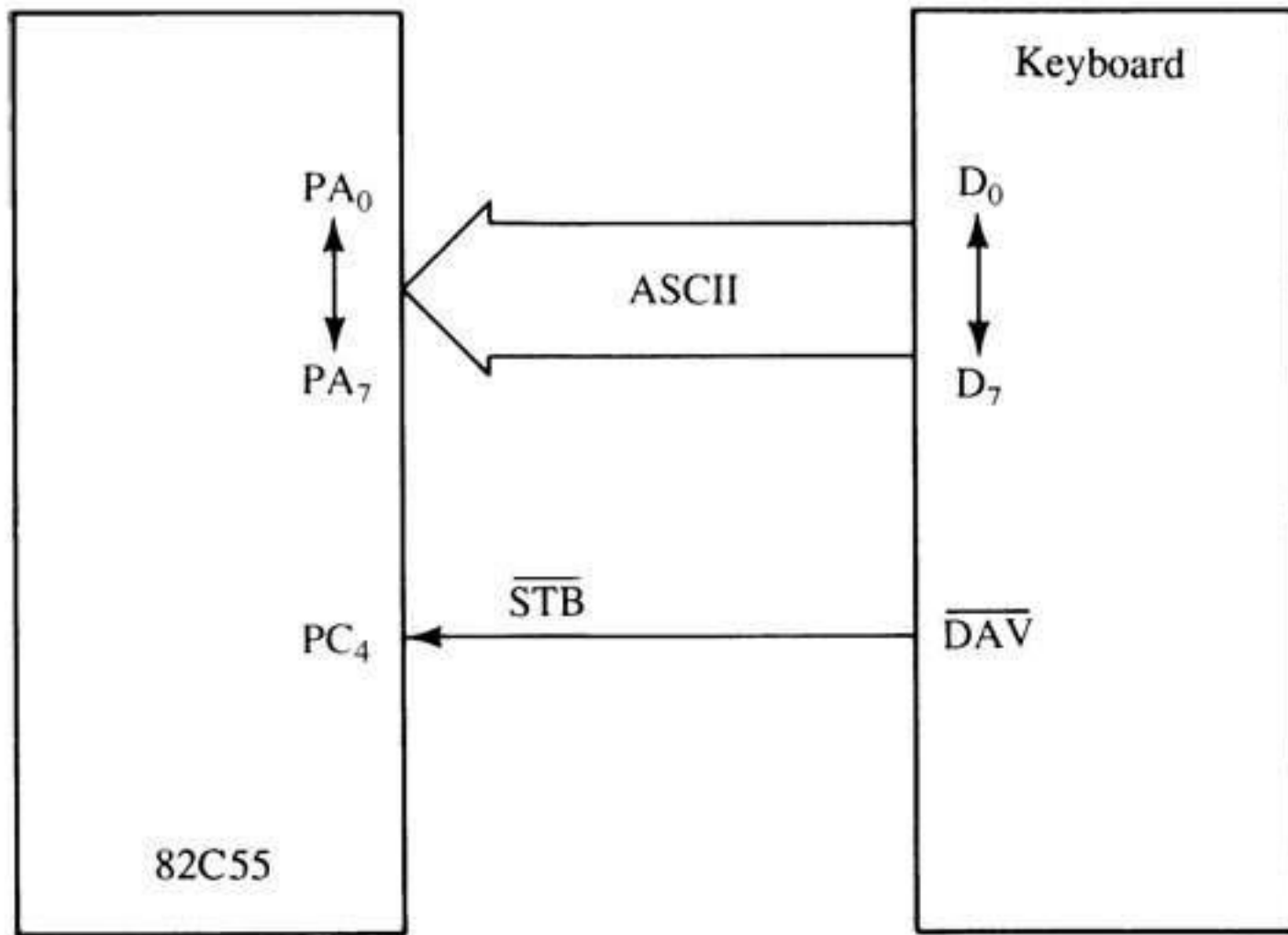

Mode 1 Strobed Output

- Fig 11–29 shows the internal configuration and timing diagram of 82C55 when operated as a strobed output device under mode 1.
- Strobed output operation is similar to mode 0 output operation.
 - except control signals are included to provide handshaking
- When data are written to a strobed output port, the **output buffer full** signal becomes logic 0 to indicate data are present in the port latch.

Figure 11–29 Strobed output operation (mode 1) of the 82C55. (a) Internal structure and (b) timing diagram.

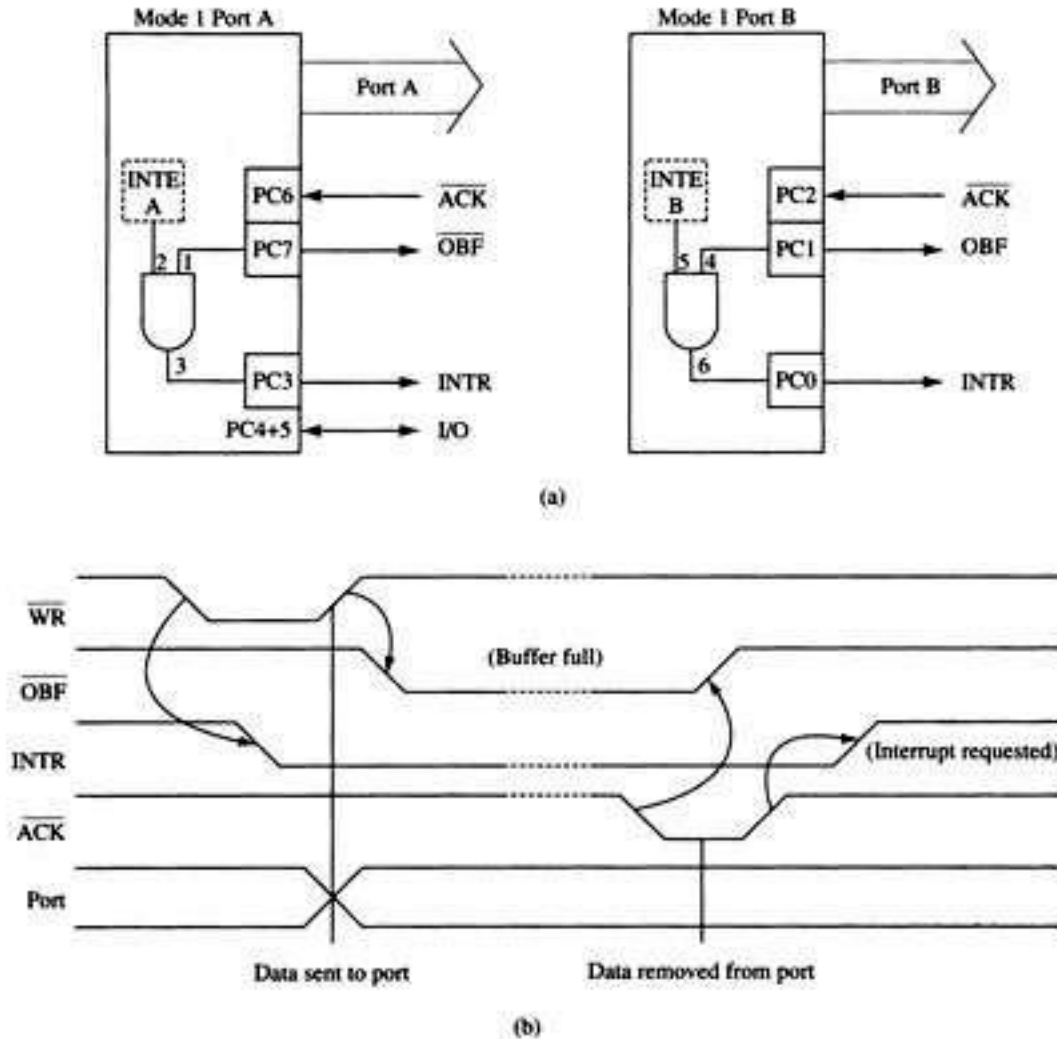

Signal Definitions for Mode 1

Strobed Output

OBF

- **Output buffer full** goes low whenever data are output (OUT) to the port A or B latch. The signal is set to logic 1 when the ACK pulse returns from the external device.

ACK

- The **acknowledge signal** causes the $\overline{\text{OBF}}$ pin to return to logic 1. The $\overline{\text{ACK}}$ signal is a response from an external device, indicating that it has received data from the 82C55 port.

INTR

- **Interrupt request** often interrupts the processor when the external device receives the data via the $\overline{\text{ACK}}$ signal. Qualified by the internal INTE (**interrupt enable**) bit.

INTE

- **Interrupt enable** is neither input nor output; it is an internal bit programmed to enable or disable the INTR pin. INTE A is programmed using PC_6 bit. INTE B is programmed using the PC_2 bit.


PC_4 , PC_5

- Port C pins PC_4 and PC_5 are general-purpose I/O pins. The bit set and reset command is used to set or reset these two pins.

Strobed Output Example

- The printer interface demonstrates how to achieve strobed output synchronization between the printer and the 82C55.
- Figure 11–30 illustrates port B connected to a parallel printer, with eight data inputs for receiving ASCII-coded data, a \overline{DS} (**data strobe**) input to strobe data into the printer, and an ACK output to acknowledge the receipt of the ASCII character.


Figure 11–30 The 82C55 connected to a parallel printer interface that illustrates the strobed output mode of operation for the 82C55.

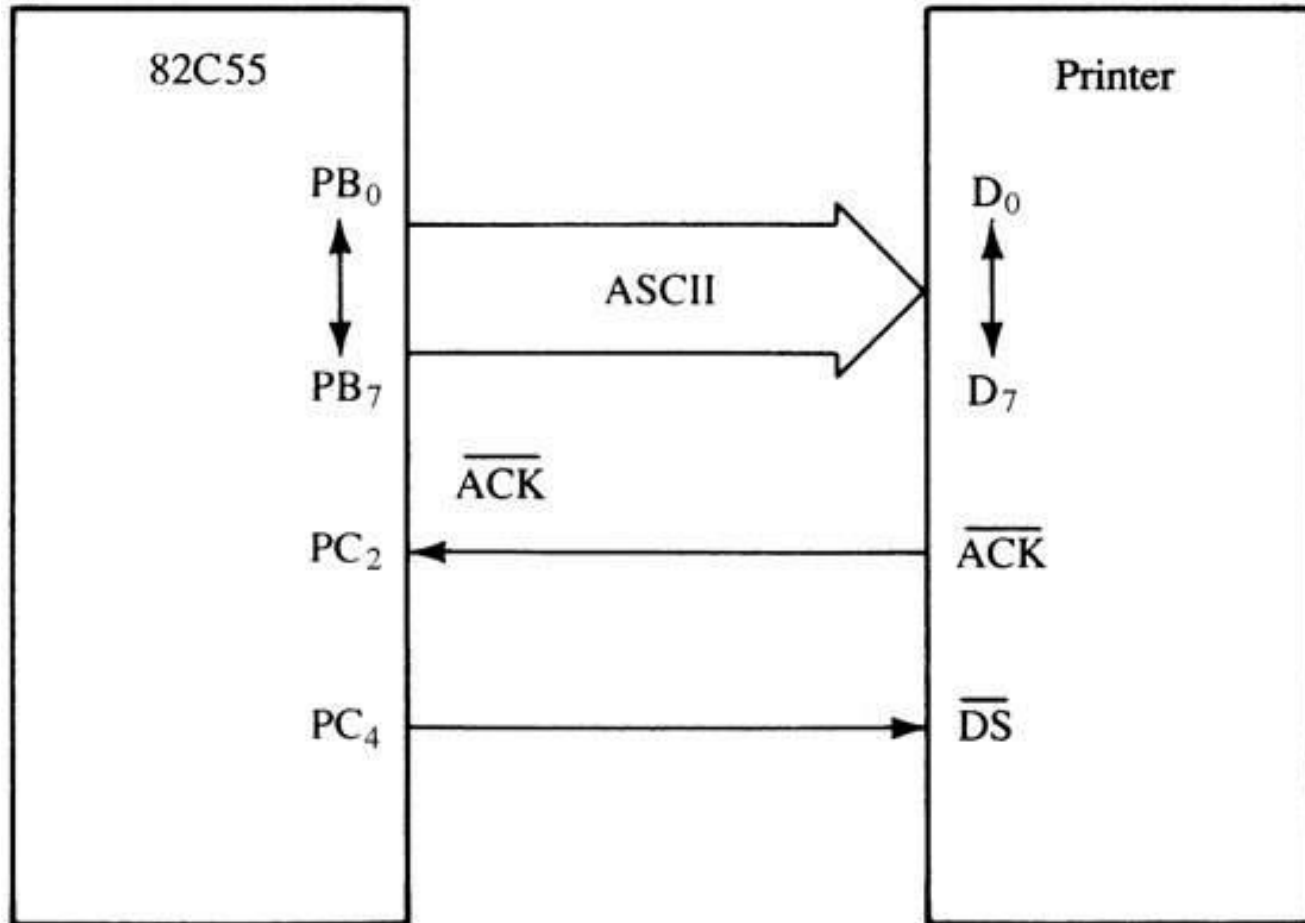

Mode 2 Bidirectional Operation

- Mode 2 is allowed with group A only.
- Port A becomes bidirectional, allowing data transmit/receive over the same eight wires.
 - useful when interfacing two computers
- Also used for IEEE-488 parallel high-speed GPIB (**general- purpose instrumentation bus**) interface standard.
- Figure 11–31 shows internal structure and timing for mode 2 bidirectional operation.

Figure 11–31 Mode 2 operation of the 82C55. (a) Internal structure and (b) timing diagram.

 

Signal Definitions for Bidirectional Mode 2

INTR

- **Interrupt request** is an output used to interrupt the microprocessor for input and output conditions.

OBF

- **Output buffer full** is an output indicating the output buffer contains data for the bidirectional bus.

ACK

- **Acknowledge** is an input that enables the three-state buffers so that data can appear on port A. If ACK is logic 1, the output buffers of port A are at their high-impedance state.

STB

- The **strobe** input loads the port A input latch with external data from the bidirectional port A bus.

PC_0 , PC_1 , and PC_2

- These pins are general-purpose I/O pins in mode 2 controlled by the bit set and reset command.

IBF

- **Input buffer full** is an output used to signal that the input buffer contains data for the external bidirectional bus.

INTE

- **Interrupt enable** are internal bits (INTE1 & INTE2) that enable the INTR pin. The state of the INTR pin is controlled through port C bits PC_6 (INTE1) and PC_4 (INTE2).

The Bidirectional Bus

- The bidirectional bus is used by referencing port A with the IN and OUT instructions.
- To transmit data through the bidirectional bus, the program first tests to determine whether the output buffer is empty.
 - if so, data are sent to the output buffer via OUT
- The external circuitry also monitors the signal to decide whether the microprocessor has sent data to the bus.

- To receive data through the bidirectional port A bus, IBF is tested with software to decide whether data have been strobed into the port.
 - if IBF = 1, data is input using IN
- The external interface sends data to the port by using the STB signal.
 - the IBF signal becomes logic 1 and data at port A are held inside the port in a latch
- When the IN executes, the IBF bit is cleared and data in the port are moved into AL.
- See Example 11–21 for a procedure.

- The INTR (**interrupt request**) pin can be activated from both directions of data flow through the bus.
- If INTR is enabled by both INTE bits, the output and input buffers both cause interrupt requests.
- This occurs when data are strobed into the buffer using STB or when data are written using OUT.

82C55 Mode Summary

- Figure 11–32 shows a graphical summary of the three modes of operation for the 82C55.
- Mode 0 provides simple I/O.
- Mode 1 provides strobed I/O.
- Mode 2 provides bidirectional I/O.
- These modes are selected through the command register of the 82C55.

Figure 11–32 A summary of the port connections for the 82C55 PIA.

		Mode 0		Mode 1		Mode 2
Port A		IN	OUT	IN	OUT	I/O
Port B		IN	OUT	IN	OUT	Not used
Port C	0	IN	OUT	INTR_B	INTR_B	I/O
	1			IBF_B	$\overline{\text{OBF}}_B$	I/O
	2			$\overline{\text{STB}}_B$	$\overline{\text{ACK}}_B$	I/O
	3			INTR_A	INTR_A	INTR
	4			$\overline{\text{STB}}_A$	I/O	$\overline{\text{STB}}$
	5			IBF_A	I/O	IBF
	6			I/O	$\overline{\text{ACK}}_A$	$\overline{\text{ACK}}$
	7			I/O	$\overline{\text{OBF}}_A$	$\overline{\text{OBF}}$

11-4 8254 PROGRAMMABLE INTERVAL TIMER


- The 8254 consists of three independent 16-bit programmable counters (**timers**).
- Each counter is capable of counting in binary or binary-coded decimal (BCD).
 - maximum allowable input frequency to any counter is 10 MHz
- Useful where the microprocessor must control real-time events.

- Usage includes real-time clocks, event counters, and motor speed/direction control.
- Timer appears in the PC decoded at ports 40H–43H to do the following:
 - 1. Generate a basic timer interrupt that occurs at approximately 18.2 Hz
 - 2. Cause the DRAM memory system to be refreshed
 - 3. Provide a timing source to the internal speaker and other devices.
- Timer in the PC is an 8253 instead of 8254.


8254 Functional Description

- Figure 11–33 shows the pin-out of the 8254, a higher-speed version of the 8253, and a diagram of one of the three counters.
- Each timer contains:
 - a CLK input which provides the basic operating frequency to the timer
 - a gate input pin which controls the timer in some modes
 - an output (OUT) connection to obtain the output of the timer

Figure 11–33 The 8254 programmable interval timer. (a) Internal structure and (b) pin-out. (Courtesy of Intel Corporation.)

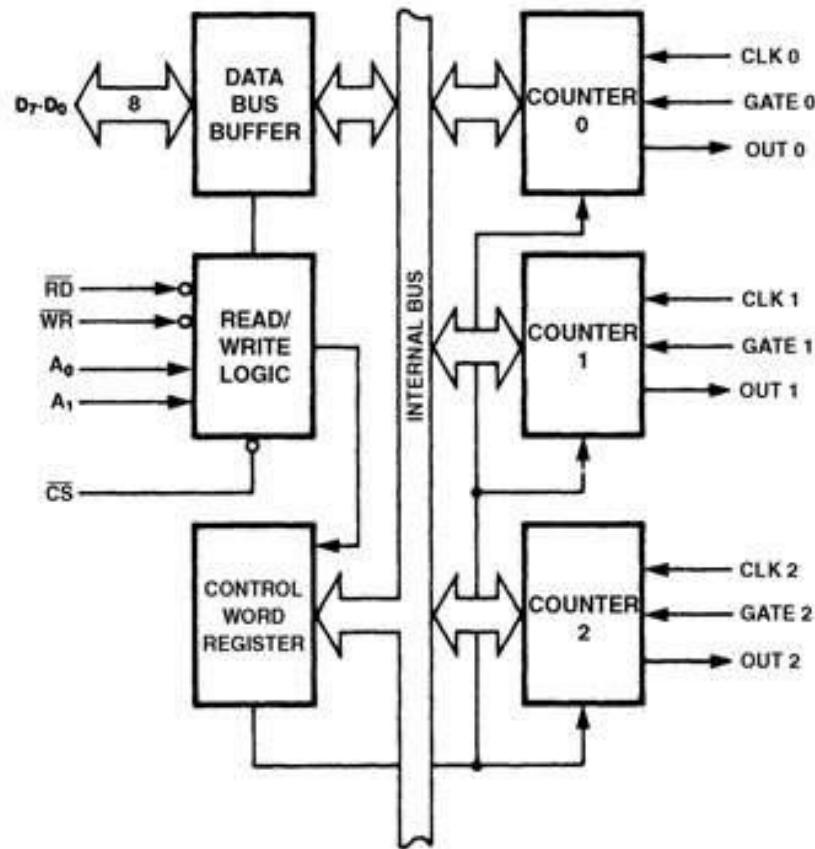

(a)

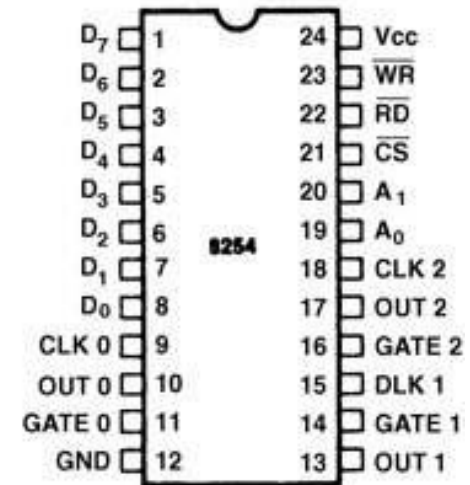

(b)

- The signals that connect to the processor are the data bus pins (D_7 – D_0), \overline{RD} , \overline{WR} , \overline{CS} , and address inputs A_1 and A_0 .
- Address inputs are present to select any of the four internal registers.
 - used for programming, reading, or writing to a counter

- Timer zero generates an 18.2 Hz signal that interrupts the microprocessor at interrupt vector 8 for a clock tick.
 - often used to time programs and events in DOS
- Timer 1 is programmed for $15\ \mu\text{s}$, used on the PC to request a DMA action used to refresh the dynamic RAM.
- Timer 2 is programmed to generate a tone on the PC speaker.

Pin Definitions for 8254

A_0 , A_1

- The **address inputs** select one of four internal registers within the 8254. See Table 11–4 for the function of the A_1 and A_0 address bits.

CLK

- The **clock** input is the timing source for each of the internal counters. This input is often connected to the PCLK signal from the microprocessor system bus controller.

CS

- **Chip select** enables 8254 for programming and reading or writing a counter.

G

- The **gate input** controls the operation of the counter in some modes of operation

GND

- **Ground** connects to the system ground bus.

OUT

- A **counter output** is where the waveform generated by the timer is available.

\overline{RD}

- **Read** causes data to be read from the 8254 and often connects to the \overline{IORC} signal.

Vcc

- **Power** connects to the +5.0 V power supply.


WR

- **Write** causes data to be written to the 8254 and often connects to write strobe IOWC.

Programming the 8254

- Each counter is programmed by writing a control word, followed by the initial count.
 - fig 11–34 lists the program control word structure
- The control word allows the programmer to select the counter, mode of operation, and type of operation (read/write).
 - also selects either a binary or BCD count

Figure 11–34 The control word for the 8254-2 timer.

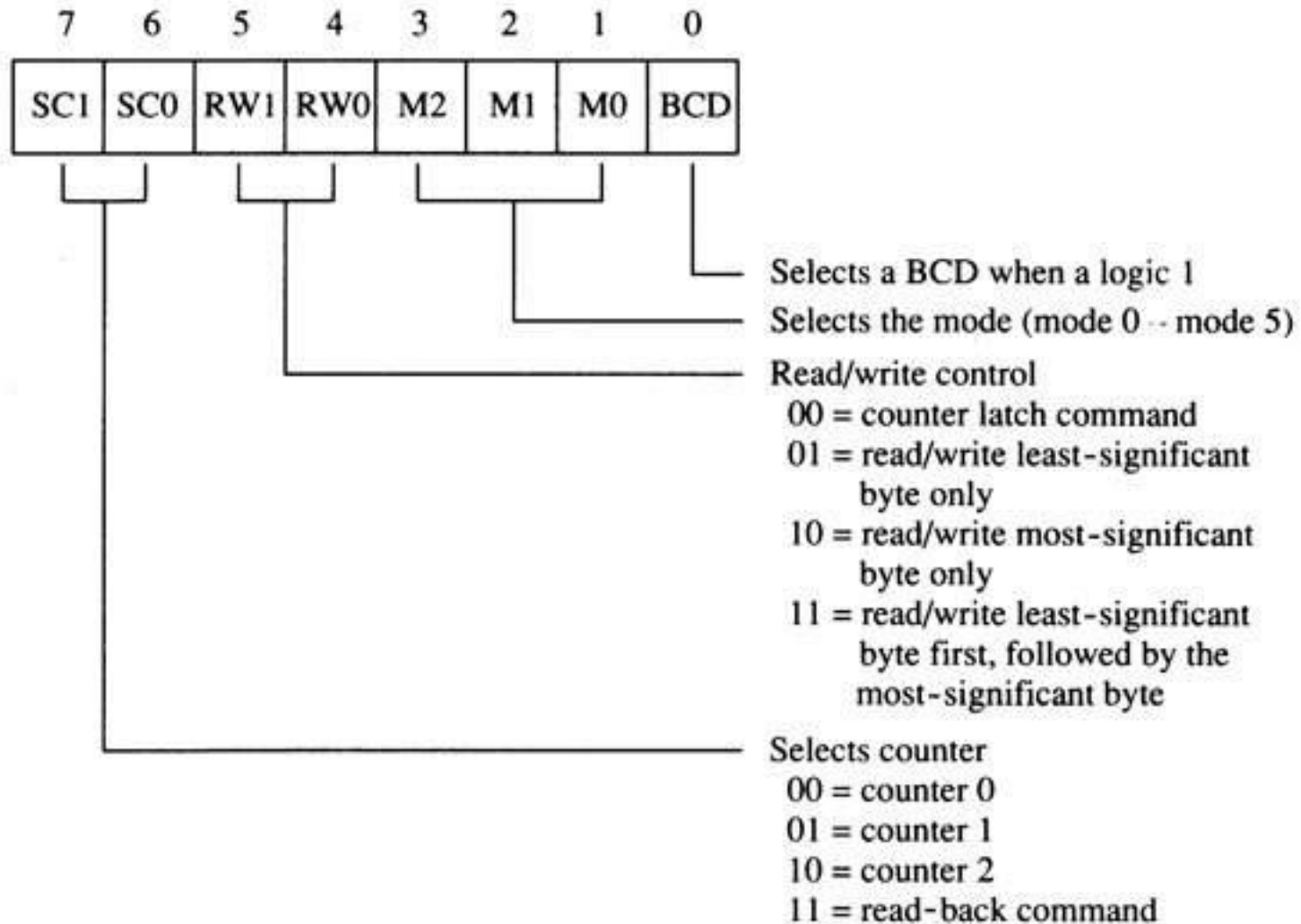

- Each counter may be programmed with a count of 1 to FFFFH; A count of 0 is equal to FFFFH+1 (65,536) or 10,000 in BCD.
- Timer 0 is used in the PC with a divide-by count of 64K (FFFFH) to generate the 18.2 Hz (18.196 Hz) interrupt clock tick.
 - timer 0 has a clock input frequency of 4.77 MHz + 4 or 1.1925 MHz
- The order of programming is important for each counter, but programming of different counters may be interleaved for better control.

Modes of Operation

- six modes (0–5) of available to each of the 8254 counters
- each mode functions with the CLK input, the gate (G) control signal, and OUT signal

 


Figure 11–35 The six modes of operation for the 8254-2 programmable interval timer. The G input stops the count when 0 in modes 2, 3, and 4.

Mode 0

- Allows 8254 to be used as an events counter.
- Output becomes logic 0 when the control word is written and remains until N plus the number of programmed counts.
- Note that gate (G) input must be logic 1 to allow the counter to count.
- If G becomes logic 0 in the middle of the count, the counter will stop until G again becomes logic 1.

Mode 1

- Causes function as a retriggerable, monostable multivibrator (one-shot).
- G input triggers the counter so it develops a pulse at the OUT connection that becomes logic 0 for the duration of the count.
 - if the count is 10, the OUT connection goes low for 10 clocking periods when triggered
- If G input occurs within the output pulse, the counter is reloaded and the OUT connection continues for the total length of the count.

Mode 2

- Allows the counter to generate a series of continuous pulses one clock pulse wide.
 - pulse separation is determined by the count
- For a count of 10, output is logic 1 for nine clock periods and low for one clock period.
- The cycle is repeated until the counter is programmed with a new count or until the G pin is placed at logic 0.
 - G input must be logic 1 for this mode to generate a continuous series of pulses

Mode 3

- Generates a continuous square wave at the OUT connection, provided the G pin is logic 1.
- If the count is even, output is high for one half of the count and low for one half of the count.
- If the count is odd, output is high for one clocking period longer than it is low.
 - if the counter is programmed for a count of 5, the output is high for three clocks and low for two clocks

Mode 4

- Allows a single pulse at the output.
- If count is programmed as 10, output is high for 10 clocking periods and low for one period.
 - the cycle does not begin until the counter is loaded with its complete count
- Operates as a software triggered one-shot.
- As with modes 2 and 3, this mode also uses the G input to enable the counter.
 - G input must be logic 1 for the counter to operate for these three modes


Mode 5

- A hardware triggered one-shot that functions as mode 4.
 - except it is started by a trigger pulse on the G pin instead of by software
- This mode is also similar to mode 1 because it is retriggerable.

Generating a Waveform with the 8254

- Fig 11–36 shows an 8254 connected to I/O ports 0700H, 0702H, 0704H, and 0706H of an 80386SX.
- The addresses are decoded by using a PLD that also generates a write strobe signal for the 8254, which is connected to the low-order data bus connections.

Figure 11–36 The 8254 interfaced to an 8 MHz 8086 so that it generates a 100 KHz square wave at OUT0 and a 200 KHz continuous pulse at OUT1.

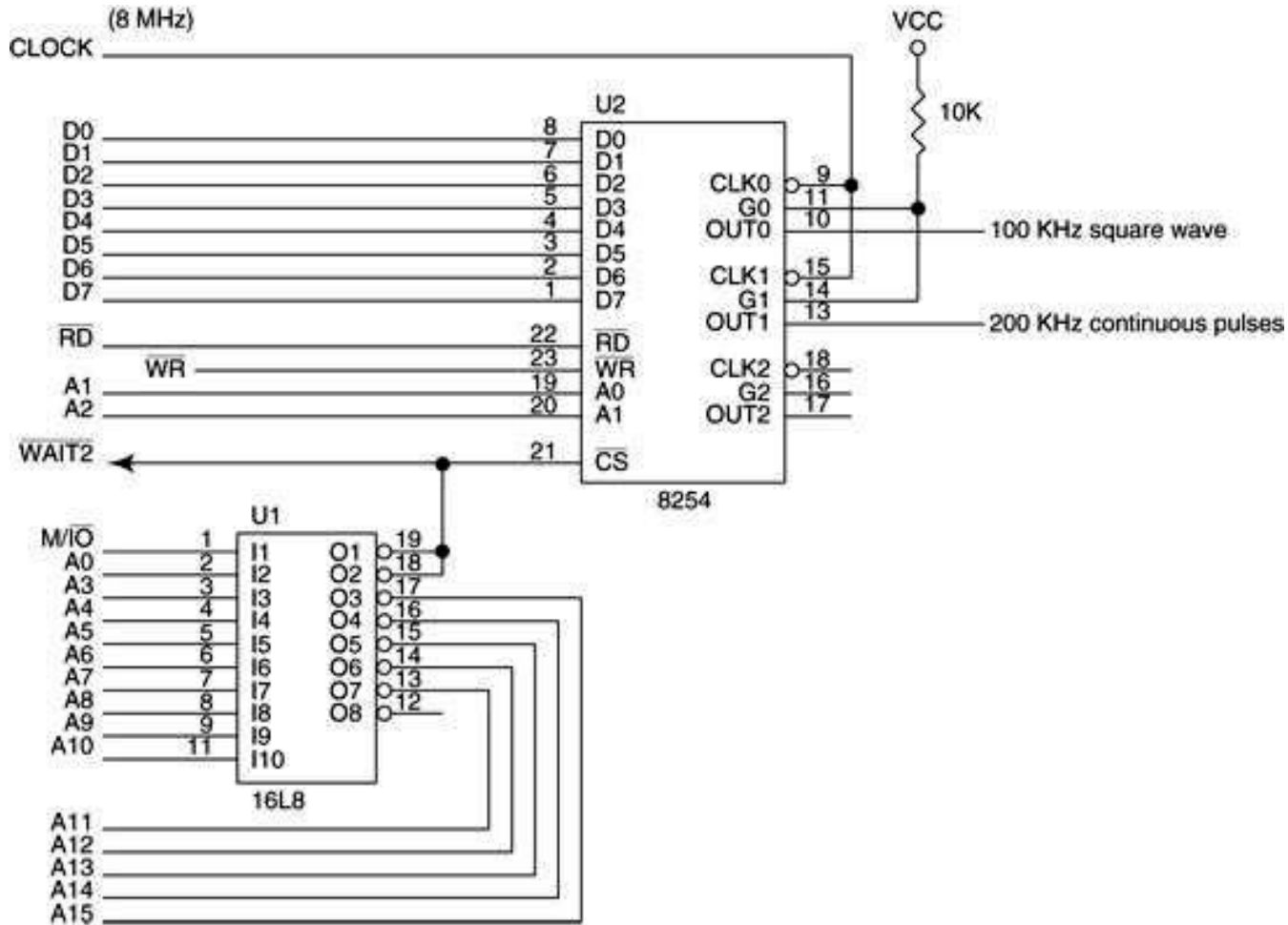


- The PLD also generates a wait signal for the microprocessor that causes two wait states when the 8254 is accessed.
- The wait state generator connected to the microprocessor actually controls the number of wait states inserted into the timing.
- Example 11–24 lists the program that generates a 100 KHz square-wave at OUT0 and a 200 KHz continuous pulse at OUT1.

Reading a Counter


- Each counter has an internal latch read with the read counter port operation.
 - the latches will normally follow the count
- If counter contents are needed, the latch can remember the count by programming the counter latch control word.
- See Figure 11–37.
 - counter contents are held in a latch until read

Figure 11–37 The 8254-2 counter latch control word.

 


- When a read from the latch or counter is programmed, the latch tracks the contents.
- When necessary for contents of more than one counter to be read at the same time, the read-back control word is used
- Illustrated in Figure 11–38.

Figure 11–38 The 8254-2 read-back control word.

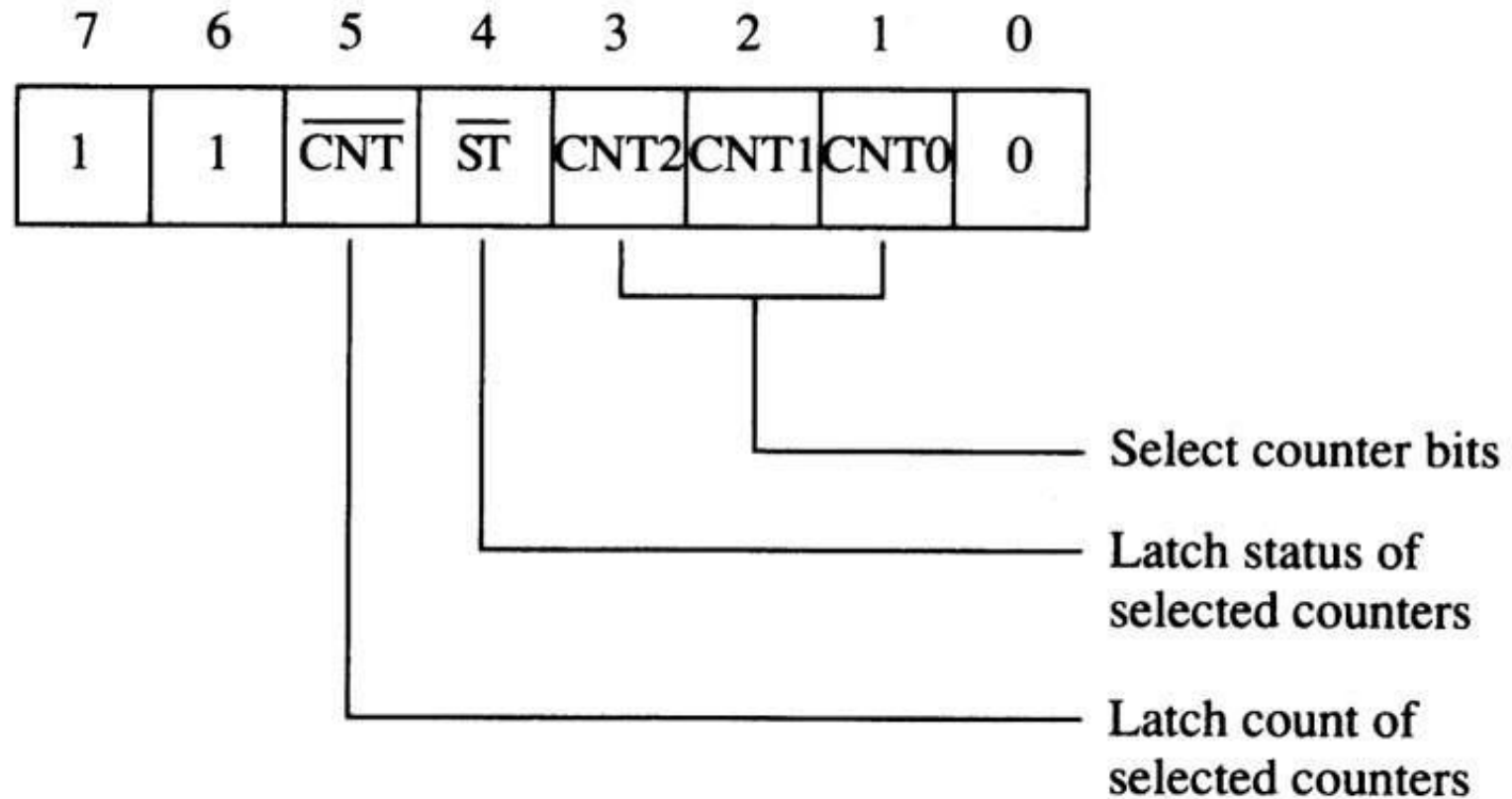

- With the read-back control word, the $\overline{\text{CNT}}$ bit is logic 0 to cause the counters selected by CNT0, CNT1, and CNT2 to be latched.
- If the status register is to be latched, then the bit is placed at logic 0.
- Figure 11–39 shows the status register, which shows:
 - the state of the output pin
 - whether the counter is at its null state (0)
 - how the counter is programmed

Figure 11–39 The 8254-2 status register.

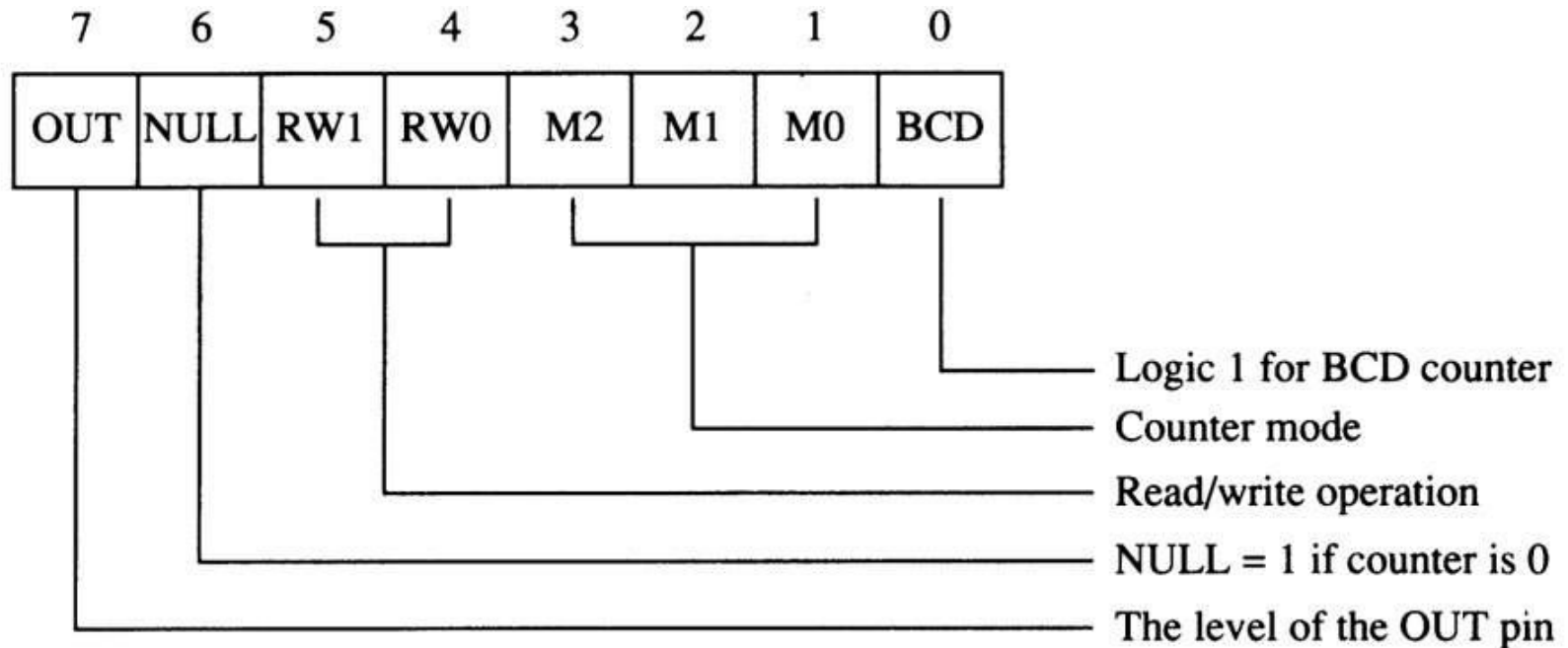

11–5 16550 PROGRAMMABLE COMMUNICATIONS INTERFACE

- National Semiconductor Corp's PC16550D is a programmable communications interface designed to connect to virtually any type of serial interface.
- 16550 is a universal asynchronous receiver/transmitter (UART) fully compatible with Intel microprocessors.

- 16550 operates at 0–1.5 M baud.
 - baud rate is bps (bits transferred per second) including start, stop, data, and parity
 - bps are bits per second; Bps is bytes per second
- 16550 also includes a programmable baud rate generator and separate FIFOs for input and output data to ease the load on the microprocessor.
- Each FIFO contains 16 bytes of storage.
- The most common communications interface found in the PC and many modems.

Asynchronous Serial Data

- Asynchronous serial data are transmitted and received without a clock or timing signal.
 - shown here are two frames of asynchronous serial data
 - each frame contains a start bit, seven data bits, parity, and one stop bit

 


Figure 11–42 Asynchronous serial data.

- Dial-up communications systems of the past, such as CompuServe, Prodigy, and America Online, used 10 bits for asynchronous serial data with even parity.
- Most Internet and BBS services use 10 bits, but normally do not use parity.
 - instead, eight data bits are transferred, replacing parity with a data bit
- This makes byte transfers of non-ASCII data much easier to accomplish.

16550 Functional Description

- Fig 11–43 shows pin-outs of a 16550 UART.
- The device is available as a 40-pin DIP (**dual in-line package**) or as a 44-pin PLCC (**plastic leadless chip carrier**).
- Two completely separate sections are responsible for data communications.
 - the receiver and the transmitter
- Because each sections is independent, 16550 is able to function in simplex, half-duplex, or full-duplex modes.

Figure 11–43 The pin-out of the 16550 UART.



- A major feature of the 16550 is its internal receiver and transmitter FIFO (first-in, first-out) memories.
- Because each is 16 bytes deep, the UART requires attention from the processor only after receiving 16 bytes of data.
 - also holds 16 bytes before the processor must wait for the transmitter
- The FIFO makes this UART ideal when interfacing to high-speed systems because less time is required to service it.

- A **simplex** system is one in which the transmitter or receiver is used by itself.
 - such as in an FM (**frequency modulation**) radio station
- A **half-duplex** system is a CB (**citizens band**) radio.
 - transmit and receive, but not at the same time
- A **full-duplex** system allows transmission and reception in both directions simultaneously.
 - the telephone is a full-duplex system

- The 16550 can control a **modem (modulator/demodulator)**, a device that converts TTL serial data into audio tones that can pass through the telephone system.
- Six pins on 16650 are for modem control: $\overline{\text{DSR}}$ (**data set ready**), $\overline{\text{DTR}}$ (**data terminal ready**), $\overline{\text{CTS}}$ (**clear-to-send**), $\overline{\text{RTS}}$ (**request-to-send**), $\overline{\text{RI}}$ (**ring indicator**), and $\overline{\text{DCD}}$ (**data carrier detect**).
- The modem is referred to as the data set and the 16550 is referred to as the data terminal.

16550 Pin Functions

A_0 , A_1 , A_2

- The **address inputs** are used to select an internal register for programming and also data transfer.
- See Table 11–5 for a list of each combination of the address inputs and the registers selected.

ADS

- The **address strobe** input is used to latch the address lines and chip select lines.
- If not needed (as in the Intel system), connect this pin to ground.
- The ADS pin is designed for use with Motorola microprocessors.

BAUDOUT

- The **baud out** pin is where the clock signal generated by the baud rate generator from the transmitter section is made available.
- It is most often connected to the RCLK input to generate a receiver clock that is equal to the transmitter clock.

CS_0 , CS_1 , $\overline{CS_2}$

- The **chip select** inputs must all be active to enable the 16550 UART.

\overline{CTS}

- The **clear-to-send** (if low) indicates that the modem or data set is ready to exchange information.
- This pin is often used in a half-duplex system to turn the line around.

D_0-D_7

- The **data bus** pins are connected to the microprocessor data bus.

\overline{DCD}

- **Data carrier detect** input is used by the modem to signal the 16550 that a carrier is present.

DTR

- **Data terminal ready** is an output that indicates that the data terminal (16550) is ready to function.

INTR

- **Interrupt request** is an output to the microprocessor used to request an interrupt (INTR=1) when the 16550 has a receiver error, it has received data, and the transmitter is empty.

DDIS

- The **disable driver** output becomes logic 0 to indicate the microprocessor is reading data from the UART.
- DDIS can be used to change the direction of data flow through a buffer.

DSR

- **Data set ready** is an input to the 16550, indicating that the modem or data set is ready to operate.

MR

- **Master reset** initializes the 16550 and should be connected to the system RESET signal.

$\overline{\text{OUT1}}$, $\overline{\text{OUT2}}$

- **User-defined output pins** that can provide signals to a modem or any other device as needed in a system.

RCLK

- **Receiver clock** is the clock input to the receiver section of the UART.

RD, $\overline{\text{RD}}$

- **Read inputs** (either may be used) cause data to be read from the register specified by the address inputs to the UART.

$\overline{\text{RI}}$

- **Ring indicator** input is placed at logic 0 by the modem to indicate the phone is ringing.

$\overline{\text{RTS}}$

- **Request-to-send** is a signal to the modem indicating that the UART wishes to send data.

SIN, SOUT

- These are the **serial data pins**. SIN accepts serial data and SOUT transmits serial data.

RXRDY

- **Receiver ready** is a signal used to transfer received data via DMA techniques.

TXRDY

- **Transmitter ready** is a signal used to transfer transmitter data via DMA.

WR, WR

- **Write** (either may be used) connects to the microprocessor write signal to transfer commands and data to the 16550.

XIN, XOUT

- These are the main **clock** connections.
- A crystal is connected across these pins to form a crystal oscillator, or XIN is connected to an external timing source.

Programming the 16550


- Programming is a two-part process & includes the initialization dialog and operational dialog.
- In the PC, which uses the 16550 or its programming equivalent, I/O port addresses are decoded at 3F8H - 3FFH for COM port 0 and 2F8H - 2FFH for COM port 2.

Initializing the 16550

- Initialization dialog after a hardware or software reset, consists of two parts:
 - programming the line control register
 - programming the baud rate generator
- The line control register selects the number of data bits, stop bits, and parity (whether even or odd, or if parity is sent as a 1 or a 0)
- Baud rate generator is programmed with a divisor that determines the baud rate of the transmitter section.

- Fig 11–44 illustrates the line control register.
- The line control register is programmed by outputting information to port 011 (A_2 , A_1 , A_0).
- The rightmost two bits of the line control register select the number of transmitted data bits (5, 6, 7, or 8).
- Number of stop bits is selected by S in the line control register.
 - if $S = 0$, one stop bit is used
 - if $S = 1$, 1.5 stop bits are used for five data bits, & two stop bits with six, seven, or eight data bits

Figure 11–44 The contents of the 16550 line control register.

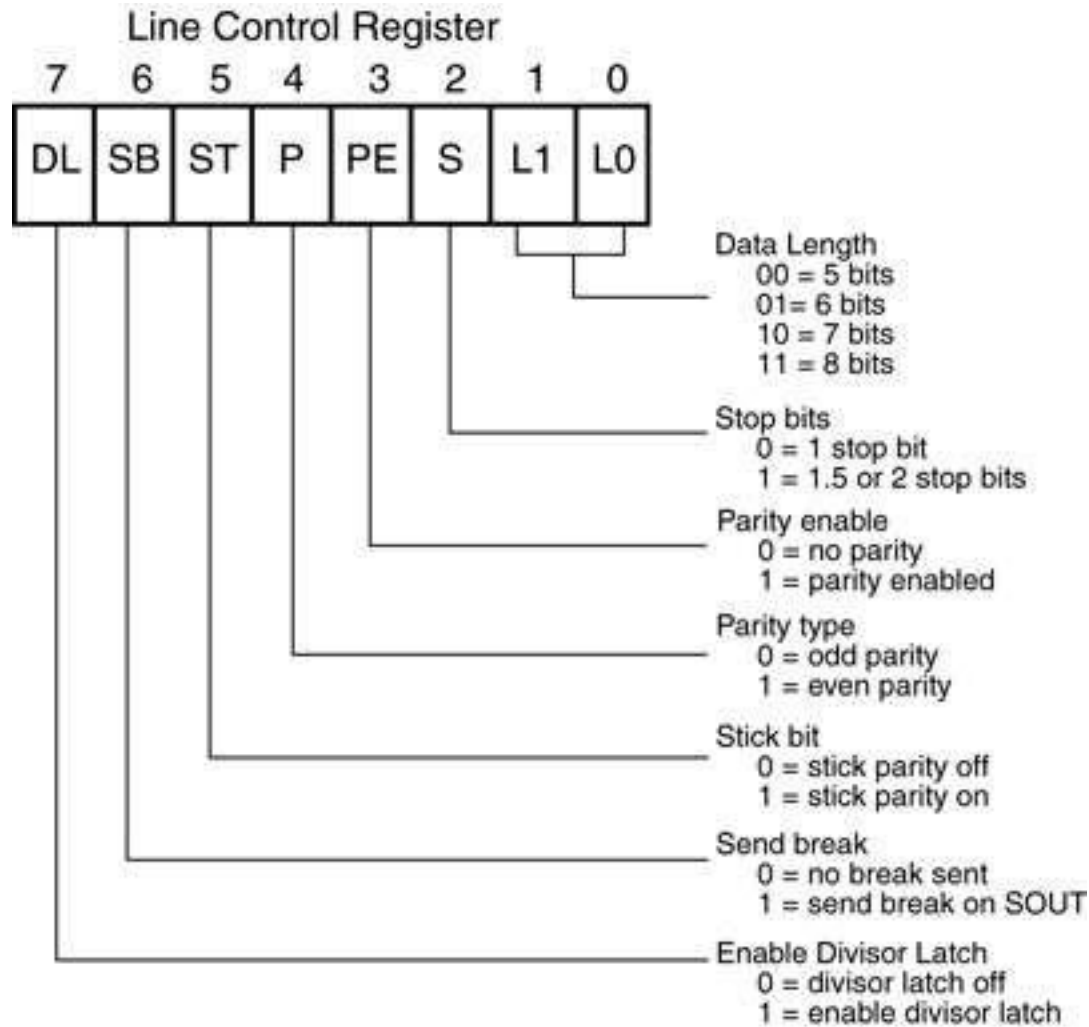


Programming the Baud Rate

- The baud rate generator is programmed at I/O addresses 000 and 001 (A_2 , A_1 , A_0).
- Port 000 is used to hold the least significant part of the 16-bit divisor and port 001 is used to hold the most significant part.
 - value used for the divisor depends on the external clock or crystal frequency
- Table 11–7 illustrates common baud rates obtainable if an 18.432 MHz crystal is used as a timing source.

Sample Initialization


- Suppose an asynchronous system requires seven data bits, odd parity a baud rate of 9600, and one stop bit.
- Example 11–24 lists a procedure to initialize the 16550 to function in this manner.
- Fig 11–45 shows the interface to the 8088 microprocessor, using a PLD to decode the 8-bit port addresses F0H through F7H.

Figure 11–45 The 16550 interfaced to the 8088 microprocessor at ports 00F0H–00F7H.

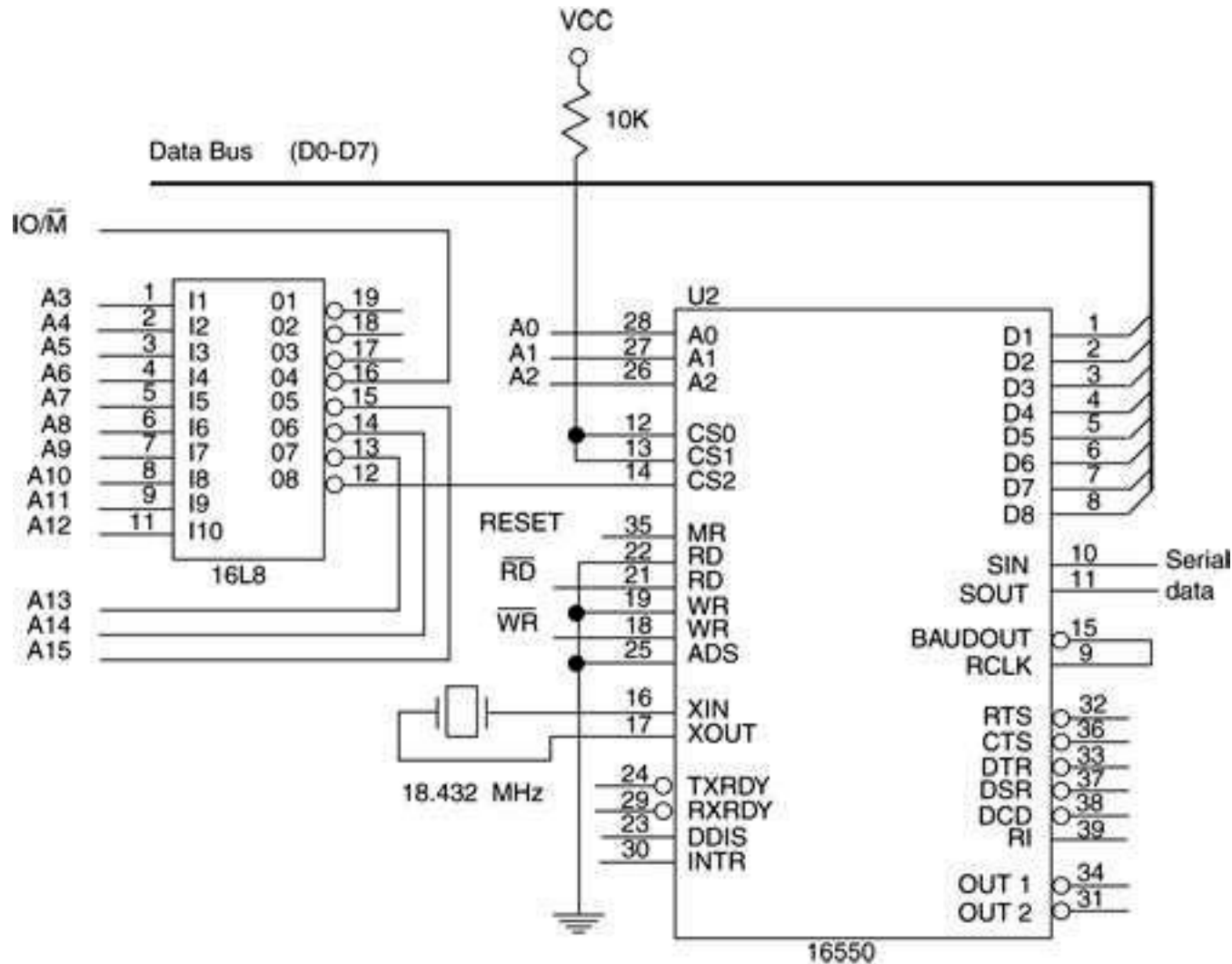

- After the line control register and baud rate divisor are programmed into the 16550, it is still not ready to function.
- The FIFO control register must still be programmed.
 - at port F2H in the circuit of Figure 11–45
- Fig 11–46 illustrates the FIFO control register for the 16550.
 - the register enables the transmitter & receiver (bit 0=1), clears the transmitter & receiver FIFOs
 - it also provides control for the 16550 interrupts

Figure 11–46 The FIFO control register of the 16550 UART.

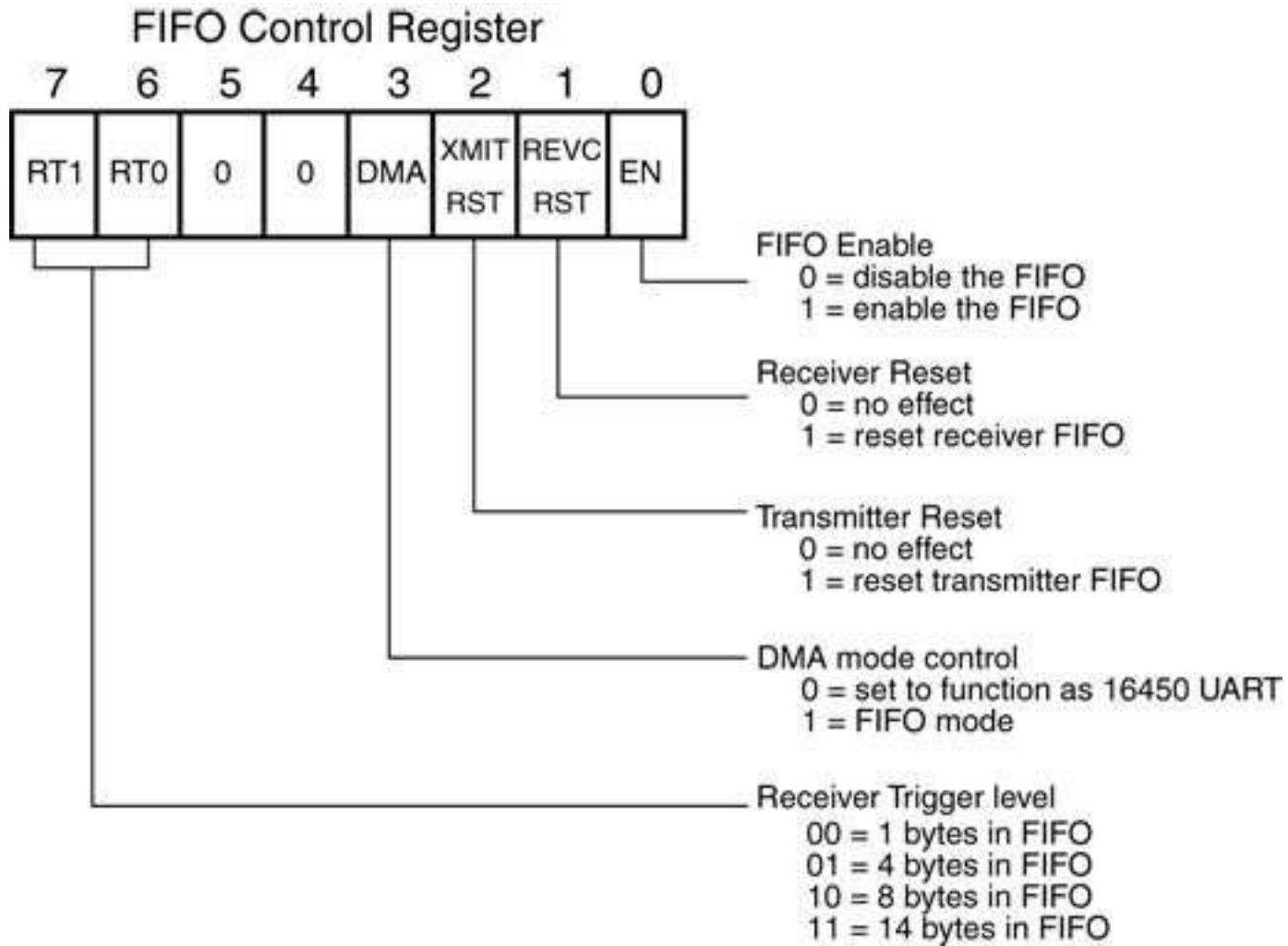


- The last section of Example 11–26 places a 7 into the FIFO control register.
- This enables the transmitter and receiver, and clears both FIFOs.
- The 16550 is now ready to operate, but without interrupts.
 - interrupts are automatically disabled when the MR (master reset) input is placed at logic 1 by the system RESET signal.

Sending Serial Data

- Before serial data can be sent or received, we need to know the function of the line status register
 - see Figure 11–47
- The line status register contains information about error conditions and the state of the transmitter and receiver.
- This register is tested before a byte is transmitted or can be received.

Figure 11–47 The contents of the line status register of the 16550 UART.

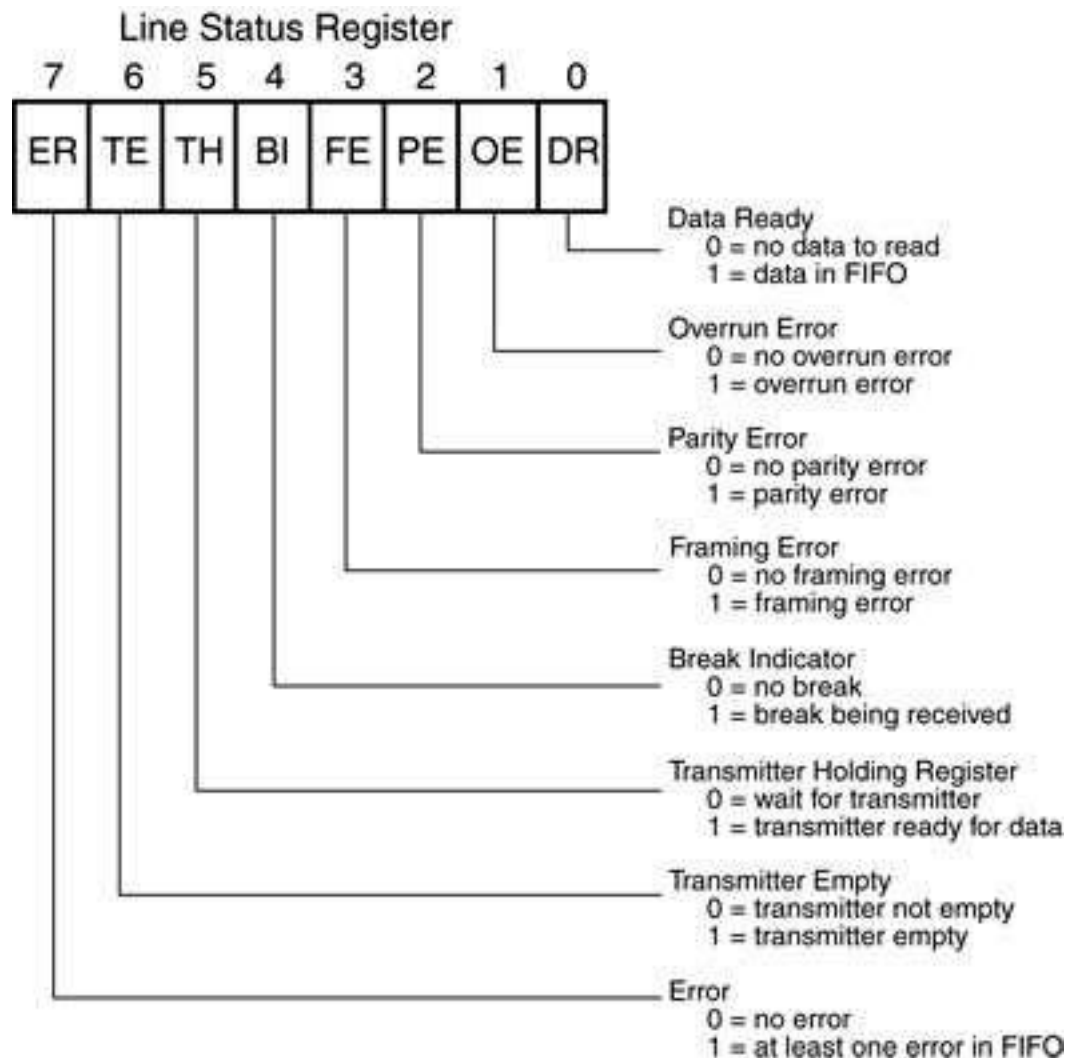

Receiving Serial Data

- To read received information from the 16550, test the DR bit of the line status register.
 - example 11–28 lists a procedure to test the DR bit to decide if the 16550 has received any data
- Upon the reception of data, the procedure tests for errors.
 - if an error is detected, the procedure returns with AL equal to an ASCII ‘?’
 - if no error has occurred, the procedure returns with AL equal to the received character

UART Errors

- Errors detected by 16550 are:
 - parity, framing, and overrun errors
- These errors should not occur during normal operation.
- A **parity error** indicates the received data contain the wrong parity.
 - if a parity error occurs, it indicates noise was encountered during reception

- A **framing error** indicates the start and stop bits are not in their proper places.
 - occurs if the receiver is receiving data at an incorrect baud rate
- An **overflow error** indicates data have overrun the internal receiver FIFO buffer.
 - occurs only if the software fails to read the data from the UART before the receiver FIFO is full

SUMMARY

- The 8086-Core2 microprocessors have two basic types of I/O instructions: IN and OUT.
- The IN instruction inputs data from an external I/O device into either the AL (8-bit) or AX (16-bit) register.
- The IN instruction is available as a fixed port instruction, a variable port instruction, or a string instruction (80286-Pentium 4) INSB or INSW.

SUMMARY

(*cont.*)

- The OUT instruction outputs data from AL or AX to an external I/O device and is available as a fixed, variable, or string instruction OUTSB or OUTSW.
- The fixed port instruction uses an 8-bit I/O port address, while the variable and string I/O instructions use a 16-bit port number found in the DX register.

SUMMARY

(*cont.*)

- Isolated I/O, sometimes called direct I/O, uses a separate map for the I/O space, freeing the entire memory for use by the program.
- Isolated I/O uses the IN and OUT instructions to transfer data between the I/O device and the micro-processor.

SUMMARY

(*cont.*)

- Memory-mapped I/O uses a portion of the memory space for I/O transfers.
- In addition, any instruction that addresses a memory location using any addressing mode can be used to transfer data between the microprocessor and the I/O device using memory-mapped I/O.

SUMMARY

(*cont.*)

- All input devices are buffered so that the I/O data are connected only to the data bus during the execution of the IN instruction.
- The buffer is either built into a programmable peripheral or located separately.
- All output devices use a latch to capture output data during the execution of the OUT instruction.

SUMMARY

(*cont.*)

- Handshaking or polling is the act of two independent devices synchronizing with a few control lines.
- This communication between the computer and the printer is a handshake or a poll.
- Interfaces are required for most switch-based input devices and for most output devices that are not TTL-compatible.

SUMMARY

(*cont.*)

- The I/O port number appears on address bus connections A7-A0 for a fixed port I/O instruction and on A15-A0 for a variable port I/O instruction (note that A15-A8 contains zeros for an 8-bit port).
- In both cases, address bits above A15 are undefined.

SUMMARY

(*cont.*)

- Because the 8086/80286/80386SX microprocessors contain a 16-bit data bus and the I/O addresses reference byte-sized I/O locations, I/O space is also organized in banks, as is the memory system.
- In order to interface an 8-bit I/O device to the 16-bit data bus, we often require separate write strobes (an upper and a lower) for I/O write operations.

SUMMARY

(*cont.*)

- The I/O port decoder is much like the memory address decoder, except instead of decoding the entire address, the I/O port decoder decodes only a 16-bit address for variable port instructions and often an 8-bit port number for fixed I/O instructions.
- The 82C55 is a programmable peripheral interface (PIA) that has 24 I/O pins that are programmable in two groups of 12 pins each (group A and group B).

SUMMARY

(*cont.*)

- The 82C55 operates in three modes: simple I/O (mode 0), strobed I/O (mode 1), and bidirectional I/O (mode 2).
- When the 82C55 is interfaced to the 8086 operating at 8 MHz, we insert two wait states because the speed of is faster than the 82C55 can handle.
- The LCD display device requires a fair amount of software, but it displays AS-CII-coded information.

SUMMARY

(*cont.*)

- The 8254 is a programmable interval timer with three 16-bit counters that count in binary or binary-coded decimal (BCD).
- Each counter is independent and operates in six different modes: (1) events counter, (2) retriggerable, monostable multivibrator, (3) pulse generator, (4) square-wave generator, (5) software-triggered pulse generator, and (6) hardware-triggered pulse generator.

SUMMARY

- The 16550 is a programmable communications interface, capable of receiving and transmitting asynchronous serial data.
- The DAC0830 is an 8-bit digital-to-analog converter that converts a digital signal to an analog voltage within $1.0 \mu\text{s}$.
- The ADC0804 is an 8-bit analog-to-digital converter that converts an analog signal into a digital signal within $100 \mu\text{s}$.